

Electronic Basic (Note on YouTube video 1-62)

24.05.2025

Pritom Saha

Khulna University of Engineering and Technology Fulbarigate, Khulna

★ Video-1:Use of a basic multimeter

#Measuring the resistance

select the ohm sign stick the probes in the right socket

The black probes always connects to the common socket

the red one will be changed depending on what we are measuring. In case of measuring voltage and resistance, the red probe will remain in the same socket.

There is awesome feature in multimeter that is continuity.when there is zero resistance between the two probes, the meter will beep. It is a great way to check the cable breaks.

#Measuring the Voltage

- Select the volt sign in (dc/ac)
- In parallel, connect the red props in positive size and the black probe in the negative side of the voltage source.

#measuring the current • the red probes is switched to the 10 ampere socket • that socket is switched to the 10 ampere because other sockets can measure only up to 500 mili amperes. if the current is higher than that the fuse may blow up. **★ Video-2: Dimming all** kind of LEDs PWM (Pulse Width Modulation) is used to control LED brightness. Lowering

voltage is inefficient and causes energy loss. Potentiometers can damage

components in high-power LEDs.

- PWM works by turning the LED on and off very fast. The duty cycle (on-time ÷ total time) controls brightness:
- 100% = fully on
- 50% = half brightness
- Lower % = dimmer light
- PWM saves energy and avoids overheating. In Arduino, the analogWrite() function easily generates PWM signals.
- PWM is a smart, efficient method for dimming LEDs using_timing, not voltage.

★ Video-3:Programming an Attiny+Homemade arduino shield #Why use ATtiny85?

- Cost-effective, smaller footprint.
- Ideal for projects with limited I/O needs (5 usable pins).

Required Materials:

- Arduino Uno.
 - ATtiny85.
- Breadboard, jumper wires.
 - 10 μF capacitor.
- Computer with Arduino IDE.

#Software Setup:

- Install Arduino IDE (version 1.0.5 recommended).
- Add ATtiny board definitions/cores (from "highlowtech.org").

4. Turn Arduino Uno into a Programmer:

- Connect Uno to computer.
- Open Arduino IDE > "ArduinoISP" sketch.
 - Upload to Uno.

#Wiring ATtiny85 to Arduino Uno (Breadboard):

- ← Arduino Pin 10 -> ATtiny Pin 1 (Reset)
- Arduino 5V -> ATtiny Pin 8 (Vcc)
- 10 μF capacitor between Uno's Reset & GND to stop auto-reset.

Programming the ATtiny85:

In Arduino IDE:

- Tools > Board > ATtiny85 (e.g., 1 MHz clock).
 - Tools > Programmer > "Arduino as ISP".
 - Write/upload sketch.
- Ignore minor "PAGEL" errors if upload completes.

Making a Programming Shield:

- Solder connections to a custom shield for repeated use.
- Eliminates breadboard rewiring.

★video-4:Arduino+Bluetooth +Android=Awesome

#Goal: Control an RGB LED using an Android phone via Bluetooth.

#Components

- Arduino Nano (brain).
- HC-05 Bluetooth module (wireless communication).
- RGB LED (color-changing light).
- Resistors (for voltage division and current limiting).

#Wiring:

- Use a voltage divider ($2k\Omega + 4.7k\Omega$ resistors) to reduce Arduino's 5V signal to 3.4V for the Bluetooth module's RX pin.

- Connect Bluetooth TX to Arduino RX directly.
- RGB LED: Common anode (+) to 5V, cathodes (-) to Arduino pins via 460Ω resistors.

#Software:

- Arduino code processes Bluetooth commands (e.g., "red" \rightarrow LED turns red).
- Use a Bluetooth terminal app (e.g., "S2 Terminal") on Android to send commands.

Lisconnect Arduino-Bluetooth TX/RX wires during code upload to avoid failure.

★ Video-5:How to Multiplex

This video explains how to control lots of LEDs (like in a matrix or cube) using an Arduino, even if it doesn't have enough pins to control each LED directly.

#Key Idea:

Use an LED matrix and multiplexing. In an LED matrix:

- LED anodes (positives) of a row are connected together.
- LED cathodes (negatives) of a column are connected together.

With multiplexing, you light up only one row at a time, rapidly switching through all rows so fast your eyes see it as steady.

#Hardware Tricks:

- Use P-channel MOSFETs (like F9540N) to switch rows on/off—they handle more current than Arduino pins.
- Use a TLC5940 driver chip to control many LED columns (it can handle 16 at once and control brightness).
- Add resistors for current limiting and to help MOSFETs work properly.

How it Works:

- 1. Arduino tells a MOSFET to power up one row.
- 2. Arduino uses the TLC5940 to choose which LEDs in that row light up.
- 3. It quickly moves to the next row, repeating this super fast for a smooth display.

#Coding:

The video uses a TLC5940 Arduino library that makes controlling the LEDs easier.

<u><u>Summary</u>:</u>

By connecting LEDs in a grid and using MOSFETs + TLC5940 with smart multiplexing, we can control lots of LEDs using just a few Arduino pins!

★ Video-6:Standalone arduino

The video explains how to remove the main chip (ATmega328P) from an Arduino Uno board and use it as a standalone circuit for smaller, more permanent projects.

#The reason

- Arduino Uno board is often too big for small projects.
- Using just the ATmega328P chip reduces size and cost.
- Allows building permanent circuits without the entire Uno board.

#Key Components & Uses:

- ATmega328P: Main controller chip runs your code.
- 16MHz Crystal: Clock sets chip's speed.
- 2x 22pF Capacitors: Stabilize the crystal's clock signal.
- 10k Ohm Resistor: Pull-up for Reset pin prevents accidental resets.
- Power (5V, GND): Powers the chip.

#Programming Options:

- 1. Swap chip to Arduino Uno to upload code.
- 2. Use Arduino Uno as programmer (TX, RX, Reset, 5V, GND).

3. Use FTDI adapter for USB-to-serial connection.

★ Video-7:Segment display

#7-Segment Displays Overview:

- Basic screens for displaying numbers (0-9) and some letters.
- Made up of 7 LED segments arranged like an "8," with an optional 8th for a decimal point.
- "Common anode" displays share the same positive pin for all LEDs.

#Pinout & Datasheets:

- Each segment (A-G, DP) is linked to a specific pin.
- Datasheets show how to wire the display correctly.

<u>***** Method 1:</u> No Arduino (Basic Counter):

- 1.Uses two chips:
 - SN74LS290: counts in binary.
 - SN74LS247: converts binary to decimal display on 7-segment.
- 2. Connect chips to display (with resistors).
- 3. Push button to make it count.

<u>← Method 2:</u> With Arduino (Multiple Digits):

- For complex displays, Arduino + SAA1064 driver chip.
- SAA1064 controls up to 4 digits using multiplexing.
- Uses I2C communication (2 wires: SDA, SCL), saving pins.
- Libraries make coding easier.

Summary:

Video explains the basics of 7-segment displays, shows how to create a simple counter with chips, and how to control more complex displays with an Arduino and a driver chip.

★ Video-8: Everything about a LEDs and current limiting registors

LED Basics

- Needs specific forward voltage (Vf)(e.g., 3.2V for green LED).
- Requires forward current (If)(~20mA) too much burns it.

#2. Why Use a Resistor?

- Limits current to protect LED.
- Always connect in series with LED.

#3. Resistor Calculation

Find resistor voltage drop:

Vresistor = Power Supply (V) – LED Vf (e.g., 5V - 3.2V = 1.8V)

Calculate resistor value:

R = Vresistor / I (e.g., $1.8V / 0.02A = 90\Omega$)

#Power Rating:Ensure resistor can handle P = Vresistor \times I (e.g., 0.036W \rightarrow use 1/4W resistor).

#Multiple LEDs

Series: Add Vf of all LEDs; calculate resistor for total drop.

Parallel (Avoid): Uneven current distribution \rightarrow LEDs may burn.

<u><u></u>summary:</u>

- 1. LEDs need specific forward voltage (Vf) and forward current (If) to operate safely.
- 2. Use a resistor in series to limit current and protect the LED.
- 3. Best to connect multiple LEDs in series, avoid using one resistor for parallel connections.

★ Video-9:Diodes and bridge rectifiers

#What a Diode Does:

Think of it like a one-way gate for electricity – it only lets current go in one direction (from anode to cathode). It stops current from going backward.

How it Works in DC Circuits:

- Protection: If you hook up a battery backward, a diode can stop the wrong current from frying your stuff.
- Voltage Drop: Diodes eat up a tiny bit of voltage (about 0.7 volts usually), so your circuit might lose a bit of power and warm up.

Making AC Power into DC (Rectification):

*Half-Wave Rectifier: Uses one diode to turn AC into DC, but it's a bit rough (only uses one half of the AC wave).

<u>*Full-Wave (Bridge) Rectifier:</u> Four diodes flip the negative part of AC into positive, giving you smoother DC.

*Adding a Capacitor: Capacitors help smooth out the final DC voltage to make it more like a battery.

<u><u>&</u>Summary</u>:

This video explains how diodes work as one-way paths for current, provides protection against reverse polarity, and describes how rectification (using diodes and capacitors) converts AC to DC, with a focus on bridge rectifiers for smoother DC output.

★ Video-10:Digital to analog converter(DAC)

#Main Components Discussed:

- Basic DAC architecture
- Concept of quantization
- R-2R ladder DAC
- PWM (Pulse Width Modulation) and low-pass filtering
- DAC0800 and I²C modules

#Key Uses of DAC:

- Converts digital data (like binary numbers) to smooth analog signals.
- Drives analog loads like speakers, sensors, or displays.
- Used in audio equipment to produce analog sound from digital data.
- Used in microcontroller projects (e.g., Arduino) for analog output.

Summary :

- The video explains why DACs are needed and how they work.
- It covers how the R-2R ladder DAC functions by using resistors to create different analog voltages from digital bits.
- Shows how buffering (using op-amps) helps drive real-world loads like speakers without distortion.
- Discusses PWM-based analog output simulation and the differences between PWM and true analog DACs.

- Also touches on practical DAC modules (like DAC0800) and how they're used in real applications.
- The video's aim is to give a clear, practical overview of DACs, especially focusing on simple explanations and real-life uses.

★ Video-11:Sending SMS with Arduino

#Components:

- TC35 GSM module
- Arduino (e.g., Uno)
- SIM card (PIN unlocked)
- Power supply (~5V for module)

#Setup:

- Insert SIM card
- Connect 5V power
- Press module's power button to connect to network (status LED blinks)

#Arduino connection:

- Connect TX/RX pins for serial communication
- Common GND connection
- Arduino can control power button pin (simulate button press in code)

Code part:

Arduino sends AT commands to module

- Enter SMS message in Serial Monitor
- Module sends SMS to target phone number (+country code, no leading zeros)



The video explains how to connect a TC35 GSM module to an Arduino using serial communication to send SMS messages. It covers hardware connections, SIM card setup, power requirements, and controlling the module via AT commands in the Arduino sketch.

★ Video-12:coils/inductors(part-1)

#Magnetic Field & Current:

- Whenever electric current flows through a wire, it generates a magnetic field around it.
- Increasing the current strengthens this field.

#Coil Shape & Core Material:

- Coiling the wire (making it into a helix) concentrates the magnetic field, making it stronger and more useful.
- Placing a ferromagnetic core (like iron) inside the coil further boosts the magnetic field.

#Inductance (L):

 Inductance is a measure of how well a coil can create and store magnetic energy.

- It's measured in Henrys (H).
- Higher inductance = better energy storage and field generation.

#Inductor Behavior in DC Circuits:

- Inductors resist sudden changes in current.
- When voltage is applied, current gradually builds up, not instantly.
- When current is stopped suddenly, the inductor tries to keep it flowing temporarily (Lenz's Law).

Energy Storage:

- Inductors store energy in the form of magnetic fields, which can be released later.
- This feature is used in circuits like boost converters to step up voltage (e.g., 3.7V to 5V USB power).

Inductive Kickback & High Voltage Spikes:

- If the current in an inductor is stopped quickly (like opening a switch), the stored energy causes a high voltage spike.
- This spike (inductive kickback) can damage sensitive components like transistors.

#Flyback Diode Solution:

- A flyback diode (or freewheeling diode) is connected across the inductor but in reverse polarity.
- It provides a safe path for the inductor's current when the switch opens, preventing harmful voltage spikes.

#Practical Uses (as mentioned in the video):

- Electromagnets (temporary magnets made with coils).
- Motors & Relays (use magnetic fields to move parts).
- Voltage Boosting Circuits (like USB chargers using boost converters).
- Protective Flyback Diodes (safeguard transistors and other parts in switching circuits).

Summary:

- Inductors create magnetic fields from electric current and store energy in those fields.
- They resist sudden current changes and can produce voltage spikes when switched off.
- Flyback diodes safely absorb these spikes, protecting sensitive electronics.

★ Video-13:coils/Inductors(part-2)

LED Protection with Inductors:

- LEDs can easily burn out if connected directly to an AC source.
- Placing an inductor in series limits the AC current, acting as a protective "cushion."
- This protective action is thanks to a unique AC property called reactance.

#What is Inductive Reactance(XL):

- Inductive reactance (XL) measures how much an inductor resists AC current flow.
- It depends on how quickly the AC changes (frequency) and the coil's ability to store energy (inductance).
- Formula: $XL = 2\pi fL$ higher frequency or stronger inductance means more current limiting.

#Energy Doesn't Just Vanish:

- Inductors don't simply turn energy into heat like resistors.
- Instead, they store it in magnetic fields and then return it to the circuit.
- This back-and-forth exchange is called reactive power.

#Phase difference:

In AC circuits, the voltage changes direction faster than the current does.

The result? The current lags behind the voltage—a mismatch in timing called phase lag.

Filtering Out the Noise

Because XL depends on frequency, inductors make great signal filters:

- Low-pass filters pass slow, low-frequency signals while blocking higher ones.
- High-pass filters do the reverse, letting faster signals through.

This helps in audio systems (bass/treble separation) and cleaning up unwanted electrical noise.

Handy Tools to Measure Inductance:

RLC meter:Inductance can be measured directly with an RLC meter.

Transistor tester:Inexpensive component testers (like transistor checkers) also measure inductance, resistance, and more.

Summary:

Inductors limit AC flow by developing reactance, which grows with frequency and coil strength.

They swap energy with the source rather than wasting it, and create a slight timing mismatch (phase shift) between current and voltage.

This makes them essential for smooth AC control, signal filtering, and protecting sensitive parts.

★ Video-14:Capacitors

#The Basics of a Capacitor:

Capacitors are like tiny energy banks — two metal plates separated by an insulating material (dielectric). When connected to a power source, one plate grabs electrons (negative), while the other sheds them (positive), forming an electric field that stores the energy.

Capacity Matters: How Much Can It Store?

- Plate Size: Bigger plates, bigger storage.
- **Gap Between Plates**: Smaller gap, more energy storage.
- **Dielectric Effect:** The insulating material (like paper, ceramic, or water) boosts the capacity.

#Key Specs: Decoding Capacitor Numbers

- Capacitance: Measured in farads (F), but usually much smaller units (μF, nF, pF).
- **Voltage Limit:** The "don't cross this line" number max voltage before it goes kaboom.
- **Polarity Check**: For some types (like electrolytic capacitors), get the positive (+) and negative (-) sides right to avoid damage.

#Circuit Roles How They Behave

In DC Circuits:

- Starts by allowing current flow to charge itself.
- Once charged, acts like an open gate (blocks DC).

←In AC Circuits:

- Lets AC flow through, but acts as a frequency filter blocks low frequencies more than high.
- Also useful for phase shifts in motors and audio signal shaping.

#Everyday Magic: Where Capacitors Help

- Fixing and tuning up electronics
- Smoothing out DC power bumps
- Filtering signals (e.g., audio tweaks)
- ✓ Timing circuits
- Power factor correction for motors

<u>**<u><u></u> <u>Summary</u>**:</u></u>

Capacitors are small components that store energy in an electric field. They smooth out power, filter signals, and work with both DC and AC circuits by letting current flow initially or selectively depending on frequency. Their capacity depends on plate size, distance, and dielectric material.

★ Video-15:Temperature Measurement(part 1)||NTC,PT100,Wheatstone Bridge

#Components:

→NTC Thermistor:

• Resistance decreases as temperature increases (non-linear).

- Cheap, commonly used in 3D printers and DIY projects.
- Requires calibration due to non-linearity.

←PT100 (RTD - Resistance Temperature Detector)

- Resistance increases with temperature (more linear than NTC).
- 100Ω at 0°C, higher accuracy, used in industrial applications.
- Small resistance changes require precise amplification (e.g., Wheatstone bridge).

├─Integrated Sensor ICs (LM35, DS18B20)

- Output voltage or digital signal directly proportional to temperature.
- Easy to interface with microcontrollers (Arduino, Raspberry Pi).
- Limited range compared to PT100 but great for simple projects.

#Measurement Techniques

→ Basic Voltage Divider:

- Pass a known current through the sensor, measure voltage drop (Ohm's Law).
- Problem: Small signal changes and offset voltage (e.g., PT100 at 0° C = 100 Ω).

←Wheatstone Bridge plus Op-Amps

- Balances offsets and amplifies tiny resistance changes.
- Requires precision resistors and careful circuit design.

Pre-Made PT100 Transmitter Modules

- Converts PT100 resistance into a standard 4–20mA current signal.
- Simplifies design—connect to a microcontroller via a shunt resistor (e.g., $250\Omega \rightarrow 1-5V$).

#Applications:

- NTC for nozzle/bed (low cost).
- PT100 for high-precision industrial machines.

Industrial Monitoring:

• PT100 with transmitters for stable, long-term accuracy.

DIY Electronics:

LM35 or DS18B20 for plug-and-play temperature sensing.

<u>Summary</u>: The video explains how to measure temperature in electronics projects using different sensors like NTC thermistors and PT100 sensors. It discusses the pros and cons of these sensors, how to read resistance changes (including using a constant current source and op-amp circuits), and how to simplify the process with pre-made PT100 transmitter modules. Finally, it shows a practical example of building a thermometer with a microcontroller and an LCD screen.

★ Video-16:Resistors

Resistors: The Circuit Traffic Managers

1 Purpose: Controlling Current Flow

Resistors act as traffic lights for electric current, ensuring the right amount flows to keep everything safe. Without them, delicate parts like LEDs could burn out from too much current. Ohm's Law (V = IR) helps figure out the ideal resistor value (in Ohms, Ω) to keep components happy.

2 Handling Heat: Power Rating

Resistors aren't just for controlling current—they also need to handle the heat they create. Their power rating (in Watts, W) tells you how much heat they can safely dissipate. If a resistor is too small for the job, it can overheat, smoke, or even break!

3 Voltage Dividers: Tapping Off Lower Voltages

Two resistors in a row can act like a simple voltage tap. This arrangement, known as a voltage divider, can create a new voltage level from a higher source—perfect for feeding sensitive parts of your circuit or shifting logic levels between devices.

4 Pull-up and Pull-down: Clear Digital Signals

When working with switches and microcontrollers (like Arduino), you don't want the pins to pick up random "floating" voltages.

- Pull-down resistor: pulls the pin to ground (0V) when the switch is open.
- Pull-up resistor: pulls the pin up to the supply voltage (like 5V) by default.

5 Current Measurement: Shunt Resistors

Tiny, low-value resistors (current shunts) can be used to measure current. By checking the small voltage across them, you can calculate how much current is flowing.

6 Special and Other Uses

- **Photoresistors, thermistors, strain gauges**: These change resistance depending on light, temperature, or pressure.
- Wire fuses: In some cases, resistors can act as basic fuses.

Summary:

Resistors are essential for controlling and managing current in circuits. They can adjust voltages, create safe connections, stabilize digital signals, measure current, and even act as sensors. Picking the right resistor and power rating keeps circuits working well and safe from damage.

★ Video-17:Oscillators||RC,LC,Crystal

#Oscillators: The Electronic Pulse Makers:

Oscillators are vital building blocks in electronics, acting like the pulse or rhythm of a circuit. These are circuits designed to continuously create signals that repeat over time, like a heartbeat or a metronome.

#Uses:

✓ Provide a timing reference for microcontrollers, processors, and clocks.

- Create signals for wireless communication (like in radios and transmitters).
- Generate regular pulses that control displays and measurement devices.
- In short, if you want anything in electronics to "tick" or "sync up," you probably need an oscillator!

Types of Oscillators

RC Oscillators – The Basic Pulse Creators

- Use resistors (R) and capacitors (C).
- The capacitor charges and discharges in a repetitive cycle through the resistor.
- As the capacitor voltage crosses certain thresholds, a transistor or chip (like the famous 555 timer IC) flips the state, starting over again.
- This simple action creates a square wave—a rapid on/off pattern.
- By adjusting the resistor or capacitor values, you can tweak the speed (frequency) of the oscillation.

LC Oscillators - The Natural Resonators

- Combine an inductor (L) and a capacitor (C) to create a natural exchange of energy.
- The capacitor stores electrical energy, while the inductor stores magnetic energy.
- This exchange sets up a smooth sine wave as energy "sloshes" back and forth.
- Because some energy leaks out, an amplifier (like a transistor) helps keep it going.
- These are great for higher frequencies (like in radio transmitters).

Crystal Oscillators - The Ultimate Timekeepers

- Use a tiny quartz crystal that vibrates at a very precise frequency when voltage is applied—thanks to the piezoelectric effect.
- This mechanical vibration is turned into an electrical oscillation that's incredibly stable—perfect for clocks and processors.
- Just like LC circuits, they rely on an amplifier and feedback loop to keep the crystal's "ringing" alive.

The Core Principles

- Resonant Frequency: The "preferred" frequency at which a circuit wants to oscillate naturally.
- Peedback: Part of the output signal is fed back to the input to keep the cycle running.
- Amplification: To overcome energy losses and keep the oscillation strong.
- **P** Recap: Who Uses Them?

Arduino & microcontrollers: for their internal clocks

Radios and wireless gear: for carrier signals

Multimeters & meters: for display refresh rates

Watches & computers: as stable timing references

Summary:

Oscillators are circuits that create repeating signals (like square or sine waves).

They're crucial for clocks, communication, and controlling timing in devices.

Types include RC (basic), LC (smooth waves), and crystal (very precise) oscillators.

★ Video-18:DC & brushless DC motor+ESC

Brushed Motors (Basics)

- These motors spin because they have stationary magnets on the outside and rotating coils inside.
- Brushes physically contact a spinning commutator to switch power in the coils, causing them to attract or repel the outer magnets that's how the motor spins.

<u>Downside:</u> brushes & commutator cause wear and need maintenance.

Brushless Motors (Why Better)

- Brushless motors ditch the physical contact no brushes or commutator!
- Instead, coils are on the stationary part (stator) and magnets on the spinning part (rotor).
- This no-contact design means less friction, more lifespan, and better efficiency.

ESC: The Brains of Brushless

- Since there's no commutator to swap power around, the ESC (Electronic Speed Controller) takes over.
- It's like a mini computer, sending power to coils in a precise, rotating sequence.
- This creates a moving magnetic field that pulls the rotor's magnets around smoothly.
- The ESC also lets you control speed by adjusting how fast it cycles power.

KV rating tells you how many RPMs the motor will spin for every 1 volt.

- Lower KV → more torque but slower speeds.
- Higher KV → faster spinning but weaker torque.

<u><u>&</u>Summary</u>:

Brushed motors spin using physical brushes and commutators to swap power in the coils, causing rotation. Brushless motors avoid these mechanical parts, using a more efficient electronic control system instead. An Electronic Speed Controller (ESC) manages the timing and sequence of power delivery, acting as the brain of the motor. The motor's KV rating shows how fast it can spin per volt, with lower KV giving more torque and higher KV giving higher speed.

★ Video-19:I2C and how to use it

#Components & Use:

- SDA (Serial Data): sends/receives data
- SCL (Serial Clock): syncs data transfer
- Only two wires needed for many devices

Why Use I2C?

- Connect multiple slave devices with just two pins
- Each device has a unique address

#Key Ideas & Steps:

- Connect SDA and SCL pins from Arduino to all devices
- Connect VCC (power) and GND to all devices
- Use $10k\Omega$ pull-up resistors to keep lines high
- Check datasheet for device's address & data bytes

#Communication:

- Master sends "start" signal
- Sends address & data bytes
- Data moves in 8-bit chunks with ACKs
- Ends with "stop" signal

#Example:

- Tuning an FM radio chip (TEA5767) using I2C.
- Finding the chip's I2C address from the datasheet.
- Sending the right data bytes to set the radio frequency (like 95.6 MHz).
- Using calculated bytes to talk to the chip and tune the radio station.

Summary:

The video explains how the I2C protocol lets you connect multiple devices (sensors, chips, etc.) to an Arduino with just two data lines (SDA and SCL). It covers wiring connections, the role of pull-up resistors, checking datasheets for device addresses and data bytes, and how communication happens in 8-bit chunks with ACK signals. Finally, it shows how to use the Arduino's Wire.h library to easily send and receive data with I2C devices.

★ Video-20:Thyristor,Triac||Phase angle control

#Key Components & Their Roles:

Thyristor: A special switch that only turns on after a gate pulse. Once on, it stays conducting until current drops below a threshold.

<u>Triac</u>: Two thyristors back-to-back to handle both halves of the AC wave.

<u>Arduino Nano:</u> Acts as a timer and controller, deciding when to fire the Triac.

Optocouplers: Safety devices to keep the Arduino's low-voltage side isolated from high-voltage AC.

<u>Full-Bridge Rectifier:</u> Converts AC to DC pulses to help detect zero crossings (when the AC wave hits zero).

<u>Potentiometer</u>: A knob to change the firing delay, controlling brightness.

<u>Light Bulb:</u> The AC load we're dimming in the demo.

#What the Video Showed:

1. Comparing Diodes & Thyristors:

- Diode = one-way street for current
- Thyristor = like a diode, but with a controllable "gate"

2. Thyristor in DC Circuits:

Gate triggers it ON.

- It stays ON (latches) as long as current is above holding current.
- Turns OFF only when main current drops.

3. Triac for Full AC Control:

- Thyristor alone won't do the trick for AC (because it's one-directional).
- Triac controls both AC halves, turning off at natural zero-crossings.

4. How Dimming Works:

- Arduino detects zero crossings with help from the rectifier and optocoupler.
- Arduino waits (delay time set by potentiometer) before triggering the Triac.
- Changing delay time = changing how much of the AC waveform reaches the light.
- ≤Short delay = more power = brighter light.
- ∠Long delay = less power = dimmer light.

5. Safety & Control:

- Optocouplers keep high voltage and low voltage parts safely apart.
- Arduino controls everything, adjusting dimming smoothly.

#The Magic of Phase Angle Control:

By adjusting the phase angle (the delay from zero crossing to firing), we control the power to the load—achieving smooth dimming.

<u></u> <u>≪summary</u>

Thyristors and Triacs can control AC power, like adjusting a light bulb's brightness.

An Arduino measures the zero crossing and fires the Triac after a set delay.

A potentiometer adjusts this delay to control brightness smoothly.

Optocouplers safely separate the high-voltage and low-voltage parts.

★ Video-21:OpAmp(Operational amplifiers)

#What is an Op-Amp?

- A small chip used to amplify signals.
- Looks like a triangle in circuit diagrams.
- Found in audio amps, sensors, filters, etc.

Power Supply:

Needs power to work.

Can be:

- Single supply: 0V and +12V
- Dual supply: -12V and +12V

Golden Rules:

Rule 1: With Negative Feedback

- If output is connected back to (-) input \rightarrow
- ➤ Op-amp adjusts output to make V+ = V-

Rule 2: Input Current

- Inputs draw almost zero current
- Useful in circuit analysis

Rule 3: No Feedback (Comparator Mode)

Acts like a switch:

- If $V+ > V- \rightarrow Output = High (close to +V supply)$
- If $V- > V+ \rightarrow Output = Low (close to -V or 0V)$

Common Amplifier Types:

*Non-Inverting Amplifier

- Input at (+), same phase output
- Gain = 1 + (Rf / Rg)

* Inverting Amplifier

- Input at (–), output flipped
- Gain = (Rf / Rin)

* AC Signal Amplification

- For single supply: add bias voltage (~½ Vcc)
- Allows AC to swing above & below midpoint

#Limitations:

- Output voltage swing: Can't exceed power supply limits
- ➤ Some "rail-to-rail" op-amps come close
- Output current: Limited
- > Can't drive high-power loads directly (e.g. big speakers)

Summary:

Op-amps follow simple rules, and with feedback resistors, can perform powerful analog tasks: amplification, filtering, comparison, and more.

★ Video-22:Transistor (BJT)as a switch

What is a BJT?

- Bipolar Junction Transistor acts like a controllable switch or amplifier.
- Has 3 terminals:
 - 1. Base (B)
 - 2. Collector (C)
 - 3. Emitter (E)
- Two types: NPN and PNP (focus is on NPN in this case).

#NPN BJT - Low-Side Switching:

- Works like an electronic gate.
- Small current into Base \rightarrow allows larger current from Collector to Emitter \rightarrow turns the load ON.
- Emitter goes to ground, load sits between power supply and Collector.

#Base Resistor (Rb) - Critical!

• Always needed to limit current into the Base.

• Without it \rightarrow too much current \rightarrow damage or destroy the BJT.

#Rb is calculated based on:

- Load current
- BJT's current gain (β or hFE)
- Input voltage controlling the Base

#Handling Different Loads:

Small Loads:

• Simple NPN BJT + correctly sized base resistor is enough.

High-Side Switching:

- Use PNP BJT when the load is grounded.
- Base must be pulled low to turn ON.

Large Loads (e.g., motors, bulbs):

- Require BJTs with higher current handling.
- May need more base current than microcontrollers (like Arduino) can supply.

#Darlington Pair:

- Two BJTs combined.
- Very high gain, needs only a small base current.
- Great for controlling large loads with weak signals.

#Final Tips:

• BJTs are useful for ON/OFF switching.

Never skip the base resistor.

Choose BJT type (NPN/PNP/Darlington) based on:

- Load size
- Control signal strength
- Circuit configuration

≤Summary:

The video explains how BJTs (especially NPN types) can be used as electronic switches.

It shows how a small current at the Base controls a larger current from Collector to Emitter.

A base resistor is essential to prevent damage to the transistor.

It also covers switching different load sizes and using Darlington pairs for bigger loads.

★ Video-23:Transistor(MOSFET) as a switch

#MOSFET: A Smart Electronic Switch

What is a MOSFET?

- A type of transistor that acts like an electronic switch
- Controlled by voltage (not current like BJTs)
- More efficient than older transistors less heat, better for big loads (like motors, LED strips)

#Basic Working Principle

Has 3 pins:

- Gate (G) controls ON/OFF
- Drain (D) connected to the load
- Source (S) connected to ground or power (depends on type)

N-Channel MOSFET:

- Turns ON when Gate voltage > Source
- Common for low-side switching (load connects to positive, MOSFET on the ground side)

#P-Channel MOSFET:

- Turns ON when Gate voltage < Source
- Used for high-side switching (MOSFET on the positive side)

#Example: Controlling an LED with Arduino

- 1. Source → connect to Ground
- 2. Drain \rightarrow to negative leg of LED
- 3. LED positive leg \rightarrow to +5V via a resistor
- 4. Gate \rightarrow connect to Arduino digital/PWM pin.
- 5. Add a $10k\Omega$ pull-down resistor between Gate and Source
- Keeps it OFF when Arduino is idle
- Prevents accidental switching from static

<u> Common Problems & Fixes</u>

Ringing / Voltage Spikes

Happens during fast switching or with motors

<u>Fix:</u> Add a small gate resistor (100–300 Ω) to slow switching just enough

Switching Losses

- MOSFET gets hot during transition (ON ↔ OFF)
- Bigger gate resistors = more heat if switching often

For high-speed/high-power: use a MOSFET driver chip

Summary:

- MOSFETs are voltage-controlled switches
- Great for everything from simple LEDs to big motors
- Add resistors to protect the MOSFET and control how fast it switches
- Know when to use N-channel vs. P-channel

★ Video-24:Stepper motors and how to use

#Stepper Motors

Stepper motors are a type of electric motor specially designed for controlled, step-by-step rotation. Unlike regular motors that spin freely, stepper motors move in very tiny, fixed

angles, allowing accurate positioning of objects. That's why they're found in machines where precision matters—like 3D printers and CNC routers.

#What Makes Them Special?

The magic of stepper motors lies in their ability to rotate in measured steps. For example, many motors take 200 tiny movements to make one full spin. That means each movement (or "step") is just 1.8 degrees!

←And the best part? Once a stepper motor stops, it holds its position tightly, almost like it's locked in place. This is incredibly useful when you want something to stay exactly where it was moved.

How They Actually Work

- Inside a stepper motor are two main components:
- A rotor, which spins and contains magnetic parts.
- A stator, which surrounds the rotor and holds several coils of wire.
- When electricity is passed through these coils in a specific sequence, they become
 magnets temporarily. These magnetic pulls guide the rotor to move step by step,
 locking into each position as it turns.

#Getting the Motor to Move Properly

You can't just plug a stepper motor into a battery and expect it to work. It needs help from a driver circuit—a small electronic component that controls which coil gets power and when. Think of it as a translator between your control signal (like from an Arduino) and the motor.

#Smoother Motion with Microstepping

A cool trick many drivers can do is something called microstepping. Instead of moving a full step each time, the motor can move in fractions of a step—like half, quarter, or even 1/16 of a step. This leads to:

- Smoother rotation
- Less vibration
- Higher precision

So instead of 200 steps per rotation, you could get up to 3200 super-fine steps—great for detailed tasks.

#How You Control It

- To get the motor turning, you send a series of electrical pulses (on-off signals) to the driver. Each pulse tells the motor to take a step (or microstep). Another wire tells the motor which direction to rotate.
- You can generate these signals using:
- A basic timer circuit like the 555 timer, or a microcontroller (like Arduino), which gives you full control over speed, direction, and step size.

Summary:

Stepper motors move in tiny, controlled angles using magnetic pulses. With help from a driver circuit, especially one that supports microstepping, these motors become powerful tools for tasks that demand precision, stability, and repeatability. Whether it's printing layers of plastic or carving designs into metal, stepper motors get the job done—one step at a time.

★ Video-25:Servos and how to use them

#Introduction to Servo Motors

Internal Components of a Servo Motor:

A servo motor is designed for precise angular movement. Its internal structure typically consists of:

- A compact DC motor responsible for generating rotation.
- A gear system that reduces rotational speed while increasing torque.
- A position sensor, often a potentiometer, which tracks the current angle of the motor shaft.
- An embedded control circuit (IC) that reads both the input signal and sensor feedback to control motor position accordingly.

#Function of Each Wire:

Standard servo motors have three wires, each serving a distinct function:

- The red wire supplies voltage (typically 5V).
- The black or brown wire serves as the ground connection (GND).
- The orange or yellow wire carries the control signal, which instructs the motor where to move.

#Understanding PWM Control:

- Servo motors operate based on Pulse Width Modulation (PWM) signals.
- A PWM signal consists of repeated electrical pulses—usually at 50 cycles per second (50 Hz). The width of each pulse determines the desired angle of rotation.

- ←A 1 ms pulse moves the servo to one extreme (approximately -90°).
- ←A 1.5 ms pulse positions the motor at the center (0°).
- ←A 2 ms pulse moves it to the opposite extreme (around +90°).

This method allows for controlled rotation within a range of roughly 180 degrees.

Methods for Controlling a Servo Motor:

★Using a Microcontroller (e.g., Arduino)

Connecting a servo to a microcontroller simplifies control. The signal wire connects to a digital output pin. Programming libraries (like Arduino's Servo library) allow the servo angle to be set directly through code commands such as write(90) to position the shaft at 90 degrees. A potentiometer can be added to adjust the angle dynamically.

★Using a 555 Timer Circuit

Servo motors can also be controlled without a microcontroller by using a 555 timer circuit. The circuit includes resistors, capacitors, and a potentiometer. Adjusting the potentiometer changes the pulse width, thereby setting the servo's position manually.

#Modifying a Servo for Continuous Rotation:

Standard servos are limited to 180° rotation. To enable full 360° continuous spinning, internal modifications are necessary:

- The mechanical stop inside the gear assembly must be removed to eliminate physical rotation limits.
- The potentiometer used for position feedback must be replaced with two equal resistors, creating a fixed voltage divider. This tricks the control circuit into believing the shaft is always centered.

Post-modification behavior:

- A 1.5 ms pulse stops the motor.
- A pulse shorter than 1.5 ms initiates rotation in one direction.
- A pulse longer than 1.5 ms causes rotation in the opposite direction.
- The speed of rotation increases as the pulse moves further from 1.5 ms.

<u>🚄 Summary:</u>

Servo motors are compact, efficient, and ideal for tasks that require precise angular positioning. They can be easily integrated into systems using microcontrollers or simple timer circuits. With internal adjustments, they can even be repurposed for continuous rotation, functioning similarly to DC motors.

★ Video-26:555 Timer IC

#555 Timer IC

What is it?

The 555 Timer is a tiny, powerful chip that can be used to create time delays, make things blink, or act like an ON/OFF switch. It's one of the most commonly used ICs in electronics because it's cheap, reliable, and very flexible. You'll find it in alarms, lights, sound generators, and many DIY circuits.

#What's Inside the Chip?

Even though the chip is small, it has several smart parts inside that work together:

<u>Voltage Divider:</u> Inside, there are three equal-value resistors that divide the supply voltage into three parts. This gives two important reference points: one at one-third and another at two-thirds of the supply voltage. These are like checkpoints that help decide when to change the output.

<u>Comparators:</u> There are two voltage comparators. These constantly check the voltage from outside (usually from a capacitor) and compare it with those reference points. Depending on what they detect, they tell the chip when to turn ON or OFF.

Flip-Flop: This part acts like a memory switch. It stores whether the output should currently be ON or OFF.

<u>Output Driver</u>: Based on what the flip-flop says, this part either gives out a HIGH (ON) signal or a LOW (OFF) signal through the output pin.

<u>Discharge Transistor:</u> This is like a smart switch that quickly removes the charge from a connected capacitor whenever needed, to reset the timing.

How Does It Work?

The 555 Timer can work in three different modes, depending on how you connect some resistors and capacitors to it from outside:

1. Monostable Mode (One-shot Timer)

In this mode, when you trigger the chip (by giving it a quick signal), the output goes HIGH for a short time and then automatically goes LOW again. It's like a timer that turns something ON for a set time and then turns it OFF by itself.

This mode is useful for things like:

• Making a light stay on for 5 seconds after pressing a button.

- Creating a short beep or delay.
- The time it stays ON depends on the values of the resistor and capacitor you connect.

2. Bistable Mode (Toggle ON/OFF)

In this setup, the 555 behaves like a flip-flop or memory switch. One input signal turns the output ON, and another turns it OFF. It stays in its current state until you tell it to change.

This is great for:

- Making a button-controlled switch.
- Turning something ON with one button and OFF with another.
- This mode doesn't need any timing components it's purely based on control signals.

3. Astable Mode (Oscillator or Blinker)

Here, the 555 works automatically without any trigger. It keeps switching the output between HIGH and LOW again and again — like a blinking light or a clock pulse.

graphis mode is useful when you want:

- LEDs to blink continuously.
- Buzzers to beep on and off.
- Signals for digital circuits.

How fast it switches and how long it stays ON or OFF depends on the resistor and capacitor values you choose. You can control both frequency (how fast it blinks) and duty cycle (how long it stays ON vs OFF).

Where Is It Used?

The 555 Timer is used in a wide range of simple and complex projects. Some common uses are:

- Delay circuits (light off after 10 seconds)
- Flashing indicators or blinkers
- Sound or tone generators
- Switch debouncing (avoiding unwanted flickering)
- Pulse generators or clock signals
- PWM (Pulse Width Modulation) control.

Summary:

The 555 Timer is like a Swiss army knife for electronics. It's tiny but can behave in many different ways — a timer, a switch, or a signal maker — all depending on how you connect a few basic components. Once you understand how it works inside, you can do a lot with it even in beginner projects.

★ Video-27: Analog to Digital Converter (ADC)

#Understanding ADCs: The Digital Eye for Analog Signals

Analog-to-Digital Converters (ADCs) allow microcontrollers and computers to interpret real-world analog inputs—like varying voltages from sensors—by translating them into digital data.

#What Does an ADC Actually Do?

An ADC converts a smooth, continuous analog signal into a series of digital numbers. This lets a microcontroller "understand" varying voltages by assigning them to fixed digital levels (usually binary).

#Two Key Factors in ADC Performance:

Sampling Rate – How Often It Checks the Signal

Definition: This tells how many times per second the ADC measures the analog input.

Nyquist Shannon Rule: To accurately capture a signal, sample it at at least twice its highest frequency.

Rule of Thumb: For good quality, sampling 10 times faster than the signal's frequency is often recommended. If you sample too slowly, you'll get a very distorted or incorrect digital version of your signal.

Practical Tip: Sampling at 10× the signal's frequency gives better precision and avoids distortion.

#Resolution - How Finely It Can Measure

Definition: This defines how many different digital values the ADC can assign to an analog signal.

Example:

- A 4-bit ADC = 2^4 = 16 levels
- A 10-bit ADC (e.g., Arduino) = 2^{10} = 1024 levels

Impact: Higher resolution means finer voltage distinctions can be detected, improving accuracy.

Inside the SAR ADC - Precision Through Guessing

SAR (Successive Approximation Register) ADCs are common in microcontrollers.

#how it works:

- 1. Takes a snapshot of the input voltage.
- 2. Begins with a rough digital guess (starting from the most significant bit).
- 3. Converts the digital guess to analog using an internal DAC.
- 4. Compares the DAC output to the actual input.
- 5. Refines the guess one bit at a time until the final digital value is determined.

Flash ADC - Speed Over Simplicity

- This is the fastest type of ADC but hardware-heavy.
- It uses many comparators, each checking if the input voltage is higher than a set reference.
- All comparisons happen at once.
- A digital encoder then translates the pattern of responses into a digital output.

A Downside: The number of comparators grows quickly with resolution.

(E.g., 8-bit flash ADC = 255 comparators!)

Summary:

An ADC is like the translator between the analog and digital world. Two things matter most:

How often it samples the signal (sampling rate)

How finely it can distinguish between voltages (resolution)

Together, they decide how faithfully an analog world is captured in digital form.

★ Video-28:IGBT and when to use them

#Understanding IGBT vs. MOSFET: A Practical Guide to Power Switching # What Are They?

Both MOSFETs and IGBTs are transistors used as high-speed electronic switches in power electronics. They control the flow of electricity by turning ON and OFF rapidly, which is critical in devices like motor controllers, power supplies, and inverters.

MOSFET (Metal-Oxide-Semiconductor Field-Effect Transistor): Ideal for fast and efficient switching at lower power levels.

IGBT (Insulated Gate Bipolar Transistor): Designed to handle much higher voltage and current, but with slower switching speed.

#How the Gate Works (Controlling the Switch)

- Both devices are activated by applying voltage to the Gate terminal.
- The Gate behaves like a capacitor it needs to be charged to turn ON and discharged to turn OFF.

• Fast switching requires a dedicated gate driver chip to quickly move charge in and out of the gate.

• An IGBT combines:

1.MOSFET-like input (voltage-driven gate),

2.with BJT-like output (strong current-handling characteristics).

.Key Differences & Performance Comparison

🚀 Switching Speed

- MOSFETs are significantly faster and suited for very high-frequency switching (above 200 kHz).
- IGBTs switch more slowly, making them suitable for medium to low frequencies.

Power Loss & Efficiency

MOSFETs: When ON, act like a small resistor — excellent efficiency at low voltages and currents due to minimal voltage drop.

IGBTs: Maintain a relatively constant voltage drop when ON — this becomes more efficient at high voltages and high currents.

At very low currents, IGBTs are less efficient and may waste more power.

Voltage & Current Handling

• IGBTs excel in high-voltage, high-current applications — making them ideal for industrial and high-power systems.

 MOSFETs are generally used where voltage and current demands are moderate to low.

Simple Rule of Thumb: When to Use What

Use a MOSFET when:

- You need high-speed switching (typically above 200 kHz).
- The system operates at lower voltage and current levels.
- You want minimal power loss at low loads.
- **Common uses:** DC-DC converters, switching power supplies, audio amplifiers.

W Use an IGBT when:

- You're switching high voltage and high current.
- The application runs at medium to low frequencies (typically below 200 kHz).
- You care more about power handling than speed.
- **Common uses:** Tesla coils, motor drives, induction heating systems.
 - <u>**Summary:</u>**</u>
 - Think "MOSFET for Speed" and "IGBT for Power"
 - Use a MOSFET when fast switching and efficiency at lower loads matter.
 - Use an IGBT when the goal is to control large amounts of power without needing ultra-fast switching.

★ Video-29:Solar Panel and Charge

#Understanding Solar Panels & Efficient Charging

| How Solar Panels Generate Electricity

Solar panels work by capturing sunlight and turning it into electrical energy. Each panel consists of many tiny units called solar cells, and while a single cell generates only a small voltage (about 0.5V), connecting many in series increases the total output to useful levels.

<u>* The Shading Problem</u>

Even partial shading — like from a leaf or passing cloud — can drastically reduce a panel's power. It's similar to a kink in a hose: block one spot, and the whole flow suffers.

Bypass Diodes: A Clever Fix

To counteract shading issues, larger panels often include bypass diodes. These allow the current to reroute around shaded sections, preventing the entire panel from being affected and keeping power losses minimal.

Finding the Power Sweet Spot

Every panel has a specific voltage-current point where it performs best, known as the Maximum Power Point (MPP). The wattage rating on a panel (like 100W) reflects output under ideal lab conditions, but real-world conditions are often less perfect.

Smarter Charging with MPPT

For battery charging, using an MPPT (Maximum Power Point Tracking) charge controller ensures the panel operates near its MPP. This results in much higher efficiency compared

to basic PWM (Pulse Width Modulation) controllers, which don't actively adjust to changing conditions.

Summary:

Solar panels are sensitive systems — shading hurts their performance, but bypass diodes help. To charge batteries efficiently, an MPPT controller is your best bet for squeezing out the most power.

★ Video-30:Microcontroller(Arduino) Timers

#Efficient Timing with Arduino: Understanding Microcontroller Timers

Timers in microcontrollers, like those in the ATmega328P (used in Arduino), are essential for executing precise time-based actions without halting the entire program. Instead of using the basic delay() function—which pauses everything—timers allow multitasking through non-blocking mechanisms.

Why Use Timers Instead of delay()?

- delay() freezes the processor, preventing it from performing other tasks (e.g., reading sensor inputs or checking button presses).
- Timers enable parallel execution—you can run timed events while still checking other conditions in your main program.

The Core Idea: What Are Hardware Timers?

• Timers are built-in counters that increment with each microcontroller clock pulse.

- You can slow down the counting using a prescaler, allowing you to handle longer time intervals.
- Timers can trigger automatic actions (via interrupts) when they reach a specific value or overflow.

Major Timer Operating Modes:

1. Basic Count-Up (Normal Mode)

- Timer starts at 0 and counts up to its max (e.g., 65535 for a 16-bit timer).
- On reaching the max, it overflows and can trigger an overflow interrupt.
- By preloading the timer with a specific value, you can precisely control when it overflows.

2. CTC Mode (Clear Timer on Compare Match)

- The timer counts up and is compared continuously with a predefined value (in a register like OCR1A).
- When the count equals the compare value, the timer resets automatically and can fire an interrupt.
- Ideal for generating repeating intervals, like blinking LEDs or timing periodic tasks.

3. Fast PWM (Pulse Width Modulation)

- Used for creating PWM signals for motor control, dimming LEDs, etc.
- The timer counts from 0 to a set TOP value.
- A compare register (like OCR1A) determines the duty cycle—how long the signal stays HIGH in each cycle.
- Frequency and duty cycle can be fine-tuned using registers like ICR1.

X How to Configure Timers in Code

You control timer behavior through a set of special-purpose registers:

- TCCR1A / TCCR1B Define the timer's operating mode and prescaler.
- OCR1A / OCR1B Hold compare values for generating match events.
- TIMSK1 Used to enable specific timer-related interrupts.

These registers give you full control over timer modes, intervals, and interrupt handling, enabling your microcontroller to work smarter—not just harder.

Summary: Why Hardware Timers Are a Game-Changer

Timers allow accurate, responsive multitasking without freezing your Arduino sketch. Whether you're blinking LEDs, generating sounds, or reading inputs while timing events, hardware timers are a crucial tool for building efficient and reliable embedded systems.

★ Video-31: Schottky Diode and Zener Diode

Quick Flashback: What Does a Normal Diode Do?

- Allows electric current to flow in only one direction (like a one-way street).
- It causes a small voltage drop (usually around 0.7V), which means some energy is lost as heat.

Commonly used to:

- Convert AC (alternating current) to DC (direct current),
- Protect circuits from damage due to reverse connection.

Schottky Diodes: Fast & Efficient Helpers

*** Key Benefits:**

1. Low Energy Loss:

Schottky diodes have a much lower voltage drop (around 0.2–0.4V).

➤ Means less heat, more efficiency — ideal for power-sensitive systems.

2. Super Fast Switching:

They can turn on and off very quickly, making them suitable for high-speed circuits like switching power supplies or DC-DC converters.

<u>A</u> Downsides:

- Not as strong in blocking high reverse voltage.
- May allow a tiny amount of current to leak in reverse (called reverse leakage current).

Zener Diodes: Voltage Guards in Reverse

***** What Makes Them Special?

- Designed to be used in reverse with a resistor.
- When reverse voltage reaches a certain point (called the Zener voltage, e.g., 5.1V), the diode starts conducting but holds the voltage steady.

Uses of Zener Diode:

- **1. Voltage Stabilizer:** Keeps output voltage stable even if input varies.
- **2. Reference Source:** Provides a fixed voltage to other components.
- **3. Overvoltage Protection:** Stops voltage from rising too high and damaging sensitive parts.

4. Signal Clipping: Can be used to cut parts of an AC signal.

Important Specs to Know:

- Zener Voltage (e.g., 5.1V, 12V)
- Power Rating (e.g., 500mW)
- Series resistor must be properly chosen to avoid overloading.

Summary:

- Schottky Diodes are great for fast switching and efficient power usage.
- Zener Diodes are perfect for holding voltage steady and protecting circuits.

★ Video-32:Relays & Optocouplers

Understanding Relay and Optocoupler Integration in Electronics

Smart Switching with Relays

Concept: A relay acts like a remote-controlled switch that uses a small current to operate a much larger one. It's ideal for controlling heavy electrical loads using low-power control signals.

Working Principle: At its core, there's a coil of wire. When electricity flows through it, the coil turns into a magnet. This magnetic field moves a mechanical lever (called an armature), which either connects or disconnects a separate circuit.

Safety Note – Flyback Diode: When the coil is turned off, the collapsing magnetic field can produce a dangerous voltage spike. To absorb this energy safely, a diode (called a flyback diode) is connected across the coil.

Pros:

- Excellent for switching large loads like motors or household appliances.
- Offers galvanic isolation—keeping the control and load circuits electrically separate for safety.

Cons:

- Mechanical parts make it slower.
- Prone to wear and tear after extended use.

<u>Q</u> Light-Based Isolation: Optocouplers

Concept: An optocoupler, or opto-isolator, uses light to pass signals between two separate electrical systems without a direct connection.

Internal Mechanism: Contains a tiny LED and a light-sensitive component (like a phototransistor) inside one package. When the LED lights up, the detector responds and triggers the output circuit.

Strength – Isolation for Protection: Since only light bridges the circuits, there's no physical electrical link—ideal for protecting low-voltage electronics like microcontrollers from high-voltage systems.

Pros:

Very effective for signal isolation.

• Faster than relays due to the lack of moving parts.

Cons:

Not built for directly switching heavy currents (unless using special types).

Why Use Both Together? A Layered Safety Approach

- In many circuits, the optocoupler first handles the signal from a low-power controller.
- That signal then activates the relay coil indirectly via the optocoupler.
- The relay then takes over to switch the high-power load.
- This combo provides dual isolation—first through light, then through physical separation—offering both signal safety and load handling power.

<u><u>&</u>Summary:</u>

The video explains how relays and optocouplers work and why they are important in electronic circuits.

Relays use a small signal to control high-power devices safely.

Optocouplers transfer signals using light, keeping circuits electrically isolated.

Together, they provide double safety when switching high-power loads from low-power controllers.

★ Video-33:Strain gauge/Load cell and how to use them to measure weight

Understanding Weight Measurement with Strain Gauges & Load Cells

1. What Is a Strain Gauge?

• A strain gauge is a thin, flexible sensor that detects stretching or compression. It's made with a special wire pattern that slightly changes its resistance when it experiences force. This resistance change is the key to detecting weight or pressure.

2. Why the Change Is Hard to Detect

 The resistance shift in a strain gauge is extremely small — too small for basic electronic boards like an Arduino to measure directly. It needs to be converted into something more noticeable.

3. Wheatstone Bridge: Turning Tiny Changes into Useful Signals

 To amplify the tiny resistance shift, we use a Wheatstone Bridge — a clever arrangement of four resistors. If one or more of them is a strain gauge, any pressure causes the bridge to produce a small voltage. This voltage is easier to measure than raw resistance.

4. How to Handle Temperature Effects

• Heat or cold can also affect resistance — even without any pressure. To cancel out these unwanted changes, we often use multiple strain gauges in the bridge (like in half-bridge or full-bridge designs). This setup improves accuracy.

5. Amplifying the Signal with an Op-Amp

 Even with the Wheatstone Bridge, the resulting voltage is still tiny. An operational amplifier (op-amp) boosts this voltage to a more usable level so it can be read by electronics without error.

6. Load Cells: A Ready-Made Pressure Sensor

A load cell is a metal device that already has strain gauges embedded in it, arranged in a Wheatstone Bridge format. When you apply weight, the load cell slightly bends, and the strain gauges inside detect that force — outputting a small voltage change.

7. HX711: The Easy Bridge Between Load Cell and Arduino

The HX711 module is a small chip made specifically for reading data from load cells. It amplifies the signal and converts the analog voltage into a highly accurate 24-bit digital value. You simply connect it to your load cell and Arduino to measure weight precisely — no complicated circuits needed.

Summary:

- Strain Gauge senses pressure through resistance changes.
- Wheatstone Bridge converts that into a measurable voltage.
- Op-Amps boost that voltage.
- Load Cells are pre-made sensors using strain gauges.
- HX711 simplifies the process for microcontrollers like Arduino.

★ Video-34:Two position controller and PID Controller

#Improving Magnetic Levitation with PID Control

1. The Challenge with Basic Levitation

The creator's earlier levitation setup was unstable—either the magnet clung to the electromagnet or dropped down. This happened because a simple on/off system couldn't maintain balance, lacking the finesse needed for smooth control.

2. Smarter Hardware for Better Stability

- To improve the design, several hardware upgrades were made:
- A more powerful electromagnet was introduced.
- A high-precision SS495A Hall effect sensor was directly attached to the electromagnet to detect the magnet's exact position.
- An Arduino microcontroller replaced the old circuit as the system's intelligent core.
- A sturdier physical frame provided mechanical stability.

3. Understanding PID Control

At the heart of the improvement lies the PID controller, a smart algorithm for maintaining balance. PID stands for:

- Proportional (P): Corrects based on the current error how far the magnet is from its desired position.
- Integral (I): Accumulates past errors to correct long-term drift from the target.
- Derivative (D): Predicts future errors by analyzing how fast the position is changing, helping to reduce overshoot and oscillation.

4. How PID Makes Levitation Work

The working loop of the system:

- The Hall sensor reads the floating magnet's position.
- Arduino compares this position with the setpoint (ideal location).
- The PID algorithm determines how much power the electromagnet should apply.
- A MOSFET receives this signal through PWM (Pulse Width Modulation) to control the electromagnet's strength.

5. Tuning the System

Getting the values for P, I, and D (called gains: Kp, Ki, and Kd) right is essential. The creator fine-tuned these through trial and error until a reasonably stable levitation was achieved. Each setup needs its own tuning due to differences in magnets and configurations.

6. Final Outcome

With PID control and proper tuning, the system showed far better levitation stability than before. While not perfect, it was a significant leap over the on/off method.

Summary:

The video explains how a DIY magnetic levitation system was upgraded for better stability using a PID controller.

It shows how the PID algorithm (Proportional, Integral, Derivative) helps maintain balance by adjusting the electromagnet's power.

An Arduino and precise Hall sensor are used to detect the magnet's position and control its movement.

Through careful tuning of PID values, the system achieves much smoother and more stable levitation than a basic on/off method.

★ Video-35:Schmitt Trigger and when to use them

Understanding Schmitt Triggers: Smart Signal Stabilizers

#The Issue with Standard Comparators

Ordinary comparators operate by comparing an input voltage to a single fixed reference voltage. While this works in theory, it becomes problematic when the input signal is noisy or changes very slowly. Under such conditions, the output may fluctuate erratically between high and low states, causing unstable or unpredictable behavior in the circuit.

Schmitt Trigger to the Rescue

A Schmitt trigger is a modified comparator specifically designed to handle noisy or slowly varying signals. What sets it apart is hysteresis—it doesn't switch output at just one threshold, but at two:

- Upper Threshold (UTP): Input must rise above this to switch output (usually from low to high).
- Lower Threshold (LTP): Input must fall below this to switch output back (high to low).

This dual-threshold mechanism helps maintain a steady output even when the input signal fluctuates near the switching point.

The Role of Hysteresis

Hysteresis introduces a buffer zone between switching points. Once the output changes, minor variations or noise near the threshold won't cause rapid toggling. This improves circuit stability and prevents false triggering.

How to Build or Use One

- **DIY Approach:** Combine an op-amp with a carefully arranged feedback resistor network to implement hysteresis.
- **Ready-to-Use Option:** Utilize integrated circuits like the 74HC14, which includes built-in Schmitt trigger inverters for convenient implementation.

Where Schmitt Triggers Shine

Switch Debouncing: Clean up the chatter from mechanical switches, delivering a solid on/off signal.

Signal Cleaning: Convert noisy analog inputs into crisp digital transitions.

Oscillator Circuits: With added RC components, a Schmitt trigger can form a relaxation oscillator, generating square wave outputs.

<u><u>&</u> Summary</u>

Schmitt triggers act as noise-resistant comparators, ideal for shaping unstable or bouncy inputs into reliable digital signals. They're essential in scenarios where input precision matters and output stability is crucial.

★ Video-36:SPI and how to use it

<u> Understanding SPI Communication with Arduino</u>

What is SPI?

SPI (Serial Peripheral Interface) is a synchronous communication protocol commonly used for fast data exchange between a microcontroller (master) and one or more peripheral devices (slaves) such as sensors, memory modules, or real-time clocks (RTCs). Unlike I2C, SPI offers higher speed at the cost of using more wires.

#Core SPI Connections

When using SPI, four main signal lines are involved:

- **SCLK (Serial Clock)** Clock signal generated by the master to coordinate data transfer timing.
- MOSI (Master Out, Slave In) Data is transmitted from the master to the slave.
- MISO (Master In, Slave Out) Data is sent from the slave back to the master.
- **CS / SS (Chip/Slave Select)** Used by the master to activate a specific slave device. Each slave requires a separate CS line.

<u>K</u> Getting Started with SPI on Arduino

Here's how to set up SPI communication with an SPI-based device like the DS3234 RTC:

1. Wiring Setup

Connect the slave device to the Arduino as follows (for Uno/Nano):

SCLK → D13

- MISO → D12
- MOSI → D11
- CS → D10 (or another digital pin)

2. Code Preparation:

- Include the SPI library.
- Set the CS pin as an output.
- Begin SPI using SPI.begin().
- Configure bit order and data mode (based on device datasheet).

3. Communicating with a Device:

- Pull CS LOW to activate the slave.
- Use SPI.transfer() to send or read bytes.
- Pull CS HIGH to end communication.

SPI vs I2C (Brief Insight)

SPI is faster but needs more wiring. I2C uses fewer wires but shares them among all devices using unique addresses. SPI requires one CS line per device but provides better speed and flexibility.

Real Example: RTC Chip

In the example shown (DS3234 RTC):

- Registers are configured through SPI.
- Time and date are set and then read back.
- Data is printed to the serial monitor.
- An oscilloscope shows how the signals behave during this process.

Summary :

The video explains how to use SPI communication with an Arduino, using a DS3234 RTC chip as an example.

It covers wiring the SPI pins, initializing the SPI library, and configuring settings.

It demonstrates sending and receiving data through SPI using the SPI.transfer() function.

Finally, it shows setting and reading time from the RTC, with signal verification on an oscilloscope.

★ Video-37:What is Impedance (AC Resistance)?

Revisiting DC Circuits: How Components Behave

Resistors (R): Always oppose current flow by converting electrical energy into heat. Their behavior remains consistent in DC—voltage and current are steady, so their effect is predictable.

Inductors (L) & Capacitors (C): In direct current (DC), these components mainly react to changes rather than steady states.

- Inductors oppose sudden shifts in current.
- Capacitors resist rapid voltage changes.

Once the DC settles, inductors behave like simple wires (short circuits), while capacitors act as open switches (breaks in the path).

AC Circuits: A Whole New Game

In alternating current (AC), both voltage and current constantly fluctuate.

Resistors (R): Continue to oppose current just like in DC. They do not care about frequency, and voltage and current rise and fall together—no phase shift.

Inductors (L): Resist current more as frequency increases. This resistance in AC is called inductive reactance (XL). At higher frequencies, inductors "push back" harder. Here, voltage leads current in phase.

Capacitors (C): Their opposition, called capacitive reactance (XC), decreases as frequency rises. That means they allow more current at higher frequencies. In this case, current leads voltage in phase.

Impedance: The Complete Picture of Opposition

- Impedance (Z) is the combined "resistance" in an AC circuit—it's the total challenge a circuit gives to current.
- It blends regular resistance (R) from resistors with reactance (XL from inductors or XC from capacitors).
- Like resistance, impedance is measured in ohms (Ω), but it's more complex because it involves phase angles and can't be added in a straight line. For simple setups, you use:

 $Z = \sqrt{(R^2 + X^2)}$, where X is either XL or XC.

Why Impedance is a Big Deal

• Knowing a circuit's impedance helps determine how much AC current will flow when a specific voltage is applied.

- It also explains how voltage and current are timed differently (phase shift), which is crucial in audio equipment, power delivery, and communication systems.
- In essence, impedance is resistance evolved—the AC version that accounts for time-based changes and component behavior.

<u>**Summary:**</u>

The video explains how resistors, inductors, and capacitors behave differently in DC and AC circuits.

It introduces the concept of impedance as the total opposition to AC current, combining resistance and reactance.

It shows how frequency affects inductors (more resistance) and capacitors (less resistance) in AC.

Finally, it explains how impedance also causes a phase shift between voltage and current.

★ Video-38:True,Reactive, Apparent and deformed power

✓ Understanding Electrical Power: The Real, the Reactive & the Result

Real (Active) Power - The Useful Energy

This is the actual power that performs useful tasks like turning motors or lighting bulbs. It's the energy consumed by devices to do real work, measured in Watts (W).

Reactive Power – The Supporting Role

Devices like motors and transformers (with coils) don't just need real power — they also rely on reactive power to create magnetic fields. This energy doesn't directly power devices but cycles back and forth between the source and load, measured in Volt-Amps Reactive (VAR). It's responsible for a phase difference between current and voltage.

Apparent Power - The Total Load

The full power drawn from the supply, combining both real and reactive components, is called apparent power. It reflects what the system seems to carry, measured in Volt-Amps (VA).

Power Factor - A Measure of Efficiency

The power factor (PF) indicates how efficiently electrical power is used. It's calculated as:

PF = Real Power / Apparent Power

A PF of 1 means all supplied power is doing useful work. A lower PF means more energy is being wasted as reactive power.

Why Reactive Power Can Be a Problem

- Although it doesn't perform useful work, reactive power still flows through the wires.
- This extra flow increases heat and energy losses in cables and equipment.
- To handle this unnecessary current, utilities need to use bulkier wires and larger transformers increasing costs.

#Improving Power Factor - What's the Fix?

• Power Factor Correction (PFC) is often achieved by adding capacitors in parallel with inductive loads (like motors).

- Why capacitors? Because they produce reactive power in a way that cancels out the inductive effect voltage leads current in capacitors, while it lags in inductors.
- The right balance can significantly reduce wasted power and bring PF closer to 1.

6 Other Reasons for Low Power Factor

It's not just coils — modern electronics (like laptop chargers) can distort the current waveform due to non-linear loads.

These distortions (called harmonics) also lower the power factor, even if there's no phase shift.

Bottom Line

Think of reactive power as necessary but unproductive effort — it helps some devices work but doesn't get the main job done. Reducing it improves overall system efficiency, saves energy, and reduces strain on the electrical infrastructure.

<u>▲Summary</u>:

The video explains the difference between true power, reactive power, and apparent power in electrical systems.

It highlights how reactive power, though not doing useful work, affects efficiency by increasing current flow.

The concept of power factor is introduced as a measure of how effectively power is used.

Finally, it shows how power factor correction (using capacitors) can reduce energy waste and improve system performance.

★ Video-39:Controlling a big LED Matrix?How shift resistors work!

#Mastering Large LED Matrices: A Smart Control Strategy

1. The Core Problem: Limited I/O Pins

When working with a large LED matrix, like a 32x12 grid (384 LEDs), one major challenge is that controlling each LED individually would require an impractical number of output pins from a microcontroller like an Arduino.

2. Understanding the Circuit: Reverse Engineering

To figure out how to control the matrix, you first need to analyze the wiring. This involves using a multimeter to trace the paths between the LEDs, connector pins, and the onboard integrated circuits (ICs), helping uncover how the matrix is internally structured.

3. Efficient LED Control with Shift Registers

The matrix uses shift register ICs (like the STP16C596) to simplify control.

How It Works: You send a stream of data bits (each bit representing an LED state) to the chip serially.

Latching Mechanism: After sending all bits, a latch signal is used to update all outputs at once, allowing the LEDs to change together.

Why It's Useful: With this, one chip can control multiple LEDs (e.g., 16), reducing the number of Arduino pins needed—just a data line, a clock, and a latch.

4. Lighting Smarter: The Role of Multiplexing

Instead of powering all 384 LEDs at the same time, the system lights up small groups in quick succession.

How It Works: Only a few rows or columns are powered at once, but these are rapidly cycled.

Persistence of Vision: This rapid switching happens so fast that to the human eye, the display appears continuous and stable.

5. Programming the Magic: Arduino in Action

The Arduino is programmed to manage all of this:

- It sends serial data to the shift registers to set which LEDs should be lit.
- It triggers the latch signal at the right moment to apply the updates.
- It handles multiplexing by cycling through sections of the matrix quickly.
- It creates visual patterns, such as displaying letters or animations, by determining the on/off state of each LED in the matrix.

<u><u><u></u> <u><u><u>Summary:</u></u></u></u></u>

This approach allows full control of a high-density LED display using minimal hardware resources. By combining shift registers for expanded output and multiplexing for efficient lighting, a microcontroller like Arduino can turn a complex matrix into a dynamic display for custom messages or animations.

★ Video-40:how safe is contactless payment? ||how does RFID&NFC work

Understanding Contactless Tech: RFID & NFC Explained

RFID - The Basics of Wireless Identification

- Radio Frequency Identification (RFID) is a technology that enables wireless data transfer between a reader and a tag (such as a card or fob).
- The reader emits radio waves through a coil antenna, forming an invisible energy field.
- When a tag enters this field, its antenna captures the energy, powering a tiny chip inside.
- This chip sends its stored data (like a unique ID) back by subtly altering the energy field a method the reader can decode.

NFC - Smart Communication for Payments

- Near Field Communication (NFC) is a more sophisticated form of RFID, optimized for short-range, secure interactions.
- Commonly used in contactless payments via phones and bank cards.
- Works only within a few centimeters, enhancing security.
- Unlike basic RFID, NFC supports two-way communication for instance, between two smartphones.
- It also follows strict security protocols to ensure safe transactions.

NIY Fun: Using RFID/NFC with Arduino

- You can integrate RFID/NFC tech into your own electronics projects using affordable modules like the RC522.
- Connect the module to an Arduino board.
- Use simple code to detect and read tag IDs.
- Applications include electronic locks, custom access systems, and smart indicators (like LEDs responding to specific tags).

Are Contactless Payments Secure?

- While basic RFID tags are minimal and lack protection (broadcasting ID to any reader), NFC used in banking is far more secure:
- Data is encrypted, making it hard to intercept or misuse.
- Only works within very close proximity to a reader.
- Limits on transaction amounts and PIN requirements add extra layers of protection.
- Tools like RFID-blocking sleeves or metal wallets can offer further safety by preventing unwanted scans.

≤Summary:

RFID is great for simple wireless identification, especially in hobby projects. NFC, on the other hand, adds security and versatility, making it the go-to choice for modern contactless payments.

★ Video-41:Does a DIY audio crossover make sense?How passive filters work?

Sound Frequency Controllers: Understanding Audio Crossovers

The Purpose of Crossovers

Speakers usually contain multiple components designed to handle different ranges of sound. For instance, woofers manage the deep bass, while tweeters handle sharp treble. A crossover is an internal circuit that divides incoming audio signals, directing bass to the woofer and treble to the tweeter. This ensures optimal sound quality and helps prevent damage to the speaker components.

The Core Components Behind Signal Splitting

Crossovers rely on a few key electronic parts to function:

Inductors (Coils): Allow low-frequency sounds to pass, filtering out higher ones — forming a low-pass filter for the woofer.

Capacitors: Pass high-frequency signals while blocking low ones, creating a high-pass filter for the tweeter.

Resistors: Often included to balance output levels, adjusting how loud each speaker component sounds.

• The Cutoff Frequency - Where Filters Take Over

Each filter is tuned to activate around a specific cutoff frequency — the point where it begins blocking or allowing signals. The frequency depends on the values of the inductor and capacitor used in the circuit, and this is where basic electronic formulas come into play.

Precision Matters: Tuning the Crossover

The video highlights the importance of proper crossover design. Manufacturers fine-tune crossovers to match the exact drivers (woofer, tweeter, etc.) used in their speakers. Swapping in a universal or generic crossover can throw off the balance and degrade audio performance.

Build Your Own: Custom Design & Testing

If you're into DIY audio projects, you can use specialized software to analyze or create custom crossovers. However, it's critical to understand the specifications of your speaker drivers — such as frequency range and sensitivity — to design something that truly works well.

<u>**▲Summary:**</u>

The video explains how audio crossovers split sound frequencies, sending bass to the woofer and treble to the tweeter for better sound quality.

It shows how components like inductors and capacitors act as filters to manage these frequencies.

Cutoff frequency is discussed as the point where filtering begins, based on component values.

It emphasizes the importance of matching crossovers to specific speaker parts for the best performance.

★ Video-42:Is it easy to create your own Transformer? Everything you need to know about Transformers!

What's the Role of a Transformer?

Transformers are devices that adjust the voltage of AC electricity. They usually take dangerous high voltages from power sources and convert them into lower, safer levels that devices like phones and laptops can safely use.

Key Components Inside a Transformer

- **Core (Iron or Ferrite):** A magnetic material (often layered steel or ferrite) that helps carry the magnetic field.
- **Primary Winding:** Coil of wire that receives the incoming high-voltage AC.
- **Secondary Winding: C**oil of wire that sends out the transformed (usually lower) voltage.

C How It All Works - The Magnetic Trick

- When AC current enters the primary coil, it creates a constantly changing magnetic field.
- This magnetic field is guided by the core to the secondary coil.
- The moving magnetic field generates a new voltage in the secondary coil this is called electromagnetic induction.
- The voltage change depends on the number of wire loops (turns) in each coil:

- ← More turns in the primary = step-down transformer (voltage goes down)
- ←More turns in the secondary = step-up transformer (voltage goes up)

Efficiency and Design Challenges

Energy Losses

Copper Losses: Heat caused by resistance in wires.

Iron Losses: Heat from the core due to eddy currents and hysteresis.

Magnetic Saturation: The core can only handle a limited magnetic field. Overloading can cause the transformer to overheat and fail.

Frequency: Why It Matters?

Traditional Transformers: Work at low frequencies (50–60 Hz), which require larger cores to handle power.

Modern Transformers: Use high-frequency AC (thousands of Hz), allowing smaller, lighter cores (often ferrite), which is why today's chargers are compact.

A Safety Above All

Dealing with mains electricity is extremely risky and can be fatal if not handled properly. Always treat high-voltage systems with caution and respect.

Summary:

Transformers adjust AC voltage using magnetism and coil turns. They're essential for powering electronics safely, but come with some energy loss and size limitations depending on frequency and load.

★ Video-43:Controlling Mechanical 7 segment Displays?How RS-485 and UART works!

Retro-Style Display Tech

Instead of glowing LEDs, this project features electromechanical 7-segment displays. Each digit is made from physical segments that mechanically flip to reveal white or black surfaces, forming numbers in an old-school yet fascinating way.

The Magic Behind the Flip

Each segment has a tiny permanent magnet, while electromagnets (powered coils) behind the scenes control their motion. By reversing current direction through the coils, the segment is flipped one way or the other—either showing or hiding it.

Built-In Memory Without Power

What makes these displays unique is their latching behavior. Once a segment flips, it stays that way—even if the power is cut. No need to constantly refresh the display, unlike LEDs or LCDs.

Multiplexing: One Controller, Many Displays

To manage several digits efficiently, the setup uses multiplexing—a time-sharing method where the controller rapidly switches between digits, updating each one in sequence. It happens so fast, our eyes perceive all the digits as being on simultaneously.

▼ Talking to the Displays: RS-485 + UART

The control board communicates over RS-485, a robust, long-distance serial communication standard. However, microcontrollers like the ESP8266 or Arduino typically use UART, a simpler protocol. A MAX485 chip acts as a translator, converting UART signals into RS-485 format.

Real-Time YouTube Subscriber Counter

As a final demo, the ESP8266 fetches live YouTube subscriber data from the internet and sends the number to the mechanical displays via RS-485. It's a clever way to turn a nostalgic display into a modern internet-connected project.

<u><u>&</u>Summary:</u>

The video showcases a retro-style mechanical 7-segment display system where physical segments flip using electromagnets and magnets. These displays latch in position even without power, unlike LEDs. It uses RS-485 communication and multiplexing for efficient control of multiple digits. Finally, an ESP8266 updates the display in real-time with live YouTube subscriber data.

★ Video-44:Improving my electric longboard with a CAN bus.what can the CAN bus do?

Synchronizing Dual Motors on an Electric Longboard Using CAN Bus Technology Issue Faced:

The electric longboard has two motors that sometimes don't start spinning simultaneously, despite receiving the same command from the remote control. This slight delay can affect performance.

Introducing CAN Bus as a Solution:

The video demonstrates how implementing a CAN Bus communication system can perfectly synchronize the motors.

What is CAN Bus?

- CAN stands for Controller Area Network.
- It's a communication protocol that allows multiple electronic components to exchange information over just two wires: CAN High and CAN Low.
- Widely used in automobiles to manage various systems such as engines, windows, and entertainment units.

Application on the Longboard:

- Both motor controllers (FSESC units) were connected via their CAN bus interfaces.
- Software settings in the VESC Tool were adjusted to enable CAN communication, assigning one controller as the master and the other as a slave.

This setup allowed the motors to start and run in perfect harmony.

Advantages of CAN Bus:

Robustness: Uses specialized voltage signals and error-checking mechanisms to ensure reliable message transmission.

Collision Avoidance: Prioritizes messages so that when multiple devices send data simultaneously, the most important message gets through without conflict.

Simplicity: Reduces wiring complexity by minimizing the number of connections needed.

Additional Features: Enabled traction control on the longboard, improving wheel grip and stability.

<u><u>&</u>Summary:</u>

By integrating CAN Bus, the project achieves flawless coordination between dual motors, enhancing performance and unlocking new capabilities like traction control, all through an efficient and reliable communication system.

★ Video-45:Building a Digital Music Player with I2S!What is I2S?

Creating a High-Quality Digital Audio Player Using I2S with ESP32

This tutorial covers how to use the ESP32 microcontroller to both play and record high-fidelity audio by leveraging the I2S communication protocol.

1. Audio Storage on MicroSD Card

Sound files such as WAVs are stored on a MicroSD card connected to the ESP32. The card communicates with the ESP32 via the SPI interface, allowing rapid data transfer to the microcontroller.

2. Ensuring Superior Sound Quality

Audio quality hinges on bit depth (like 16-bit for finer sound detail) and sampling rate (e.g., 44.1 kHz, which dictates how frequently the sound is sampled). Higher values in these parameters mean clearer, more precise audio.

3. Overcoming ESP32's Built-in DAC Limitations

The ESP32's internal DAC outputs only 8-bit audio, which degrades the quality of higher-bit sound files. To deliver true 16-bit audio, the video introduces an external I2S amplifier module (e.g., MAX98357A) that handles digital audio signals for better sound fidelity.

4. Understanding I2S Protocol

I2S (Inter-IC Sound) is a specialized communication interface designed for transmitting digital audio between devices. It typically uses three key signals:

Word Select (WS/LRCK): Indicates if the current audio data is for the left or right stereo channel.

Serial Clock (SCK/BCLK): Synchronizes data timing, with speed varying based on audio quality settings.

Serial Data (SD/DIN/DOUT): Carries the actual digital audio stream (bits).

This protocol is highly efficient for high-quality audio transfer.

5. Practical Implementation with ESP32

Microphone Input: Demonstrates connecting an I2S digital microphone (such as the INMP441) to capture sound input, with the ESP32 mapping I2S signals to configurable GPIO pins.

Speaker Output: Shows wiring the I2S amplifier to the ESP32 to play audio files stored on the MicroSD card through speakers, utilizing Arduino libraries for I2S handling and audio decoding.

To achieve high-quality audio on the ESP32, use a MicroSD card with SPI for fast storage access and an external I2S DAC/amplifier for playback, or an I2S microphone for input. The I2S protocol is specifically designed to efficiently transfer digital audio, making it ideal for this purpose.

★ Video-46:Does this old induction motor still work? ||How do Asynchronous Motor work?

<u>Understanding Induction Motors: A Simplified Breakdown</u>

1. The Basics – What Makes Them Different?

Induction motors, commonly found in both industrial setups and household appliances, differ from motors like DC or brushless motors. Instead of permanent magnets, they typically use a "squirrel cage" rotor made of conductive metal bars. Their stator (the stationary part) houses multiple wire windings.

2. Powering the Spin - The Role of 3-Phase AC

When 3-phase alternating current flows through the stator windings, it creates a rotating magnetic field.

This magnetic field induces currents in the rotor's metal bars.

In turn, these induced currents generate their own magnetic field within the rotor.

The interaction between these two magnetic fields results in a rotational force that causes the rotor to spin, effectively trying to "catch up" with the stator's field.

3. Why It's Called "Asynchronous"

Unlike synchronous motors, the rotor in an induction motor never fully matches the speed of the stator's rotating field.

It always lags slightly behind — a difference known as "slip."

This slip is crucial, as it's what allows the rotor currents to be induced and the motor to generate torque.

4. Motor Connections - Star and Delta Explained

Each motor has three coil sets, and how they're connected matters.

- **Star (Y):** Used when the supply voltage is high (e.g., 400V); each coil gets a reduced voltage (e.g., 230V).
- **Delta** (Δ): Used when the supply voltage matches the motor's rated coil voltage.

The terminal box of the motor allows you to choose between these configurations based on the power supply and motor specifications.

5. Running on Single-Phase Power

Some versions are designed for single-phase supply, like those in water pumps.

They use a capacitor to create a phase shift in one coil, simulating a rotating field to get the motor started and running — though it's less efficient than 3-phase operation.

6. Key Benefits

- Sturdy and durable design
- Simple construction
- Cost-effective
- Easily powered by standard 3-phase electrical grids without needing advanced controllers

<u>A Important Safety Reminder</u>

Dealing with high voltage (e.g., 230V or 400V) is dangerous and can be fatal. Any work on such systems should be handled only by trained and certified professionals.

Summary:

- The video explains how asynchronous (induction) motors work by using a rotating magnetic field from the stator to induce current in the rotor.
- This induced current creates a magnetic field that interacts with the stator's field, causing the rotor to spin.
- The motor operates slightly slower than the magnetic field (called "slip") to generate torque.
- It also covers wiring methods (Star/Delta), single-phase operation with capacitors, and key safety warnings.

★ Video-47:Building a Tube Amp!Does it produce better audio quality though?

Understanding the Appeal of Tube Amplifiers - EB#47 Insights

1. Vacuum Tubes: A Blast from the Past

Vacuum tubes, especially triodes, are a legacy technology from the early 20th century. Despite being outdated by modern standards, they remain relevant in audio applications due to their unique sound characteristics.

2. Basic Function of a Triode

A triode consists of three main parts: a heated cathode, a control grid, and an anode (plate). The heater warms the cathode, causing it to emit electrons. These electrons are drawn toward the positively charged anode. The control grid, placed between the cathode and anode, regulates this flow. A small input voltage on the grid can control a much larger output signal — this is how amplification occurs.

3. The Modern Hybrid Approach

Most commercial tube amplifiers today aren't fully analog. The vacuum tubes are usually used in the pre-amp stage, primarily to shape the tone. The heavy lifting — the actual power amplification — is often handled by modern integrated circuits like op-amps and efficient Class-D amplifiers.

4. What Makes the "Tube Sound" Special?

Colorful Distortion: Tubes add a natural-sounding distortion that many listeners describe as warm or musical.

Gentle Clipping: Unlike transistors, which clip signals sharply and harshly when overloaded, tubes do so more gradually, leading to a smoother sound.

Reduced Harsh Harmonics: There's a belief that tubes produce fewer unpleasant high-frequency artifacts when pushed hard.

5. Limitations of Tube Technology

High Operating Voltages: Tubes typically require high voltages (around 100–150V) to function.

Heat and Power Inefficiency: They consume more power due to the heating element and release significant heat, making them less efficient than solid-state components.

6. Tubes vs. Transistors: A Technical Trade-off

Transistors outperform tubes in efficiency, linearity, and practicality. They operate at lower voltages and produce cleaner amplification. However, they lack the subtle imperfections that give tube amps their unique sonic charm — which is why many audiophiles still gravitate toward tube-based gear for listening experiences, especially in the pre-amp stages.

The video explains why vacuum tube amplifiers are still popular despite being outdated. It shows how triodes work to amplify signals and why their distortion creates a warm, pleasing sound. Most modern tube amps use tubes mainly for pre-amp stages while relying on efficient transistors for power. Though less efficient, tubes are valued for their unique audio character.

★ Video-48:The best protection for your circuits! Here is why they are awesome!

Smart Power Protection for Electronics: Why eFuses Are a Game-Changer

When designing or building electronics—whether for yourself or others—power safety is crucial. Here's a simplified breakdown of how to keep your circuits safe, and why eFuses are such a powerful solution.

Name of the Projects of the Project o

For DIY electronics like walkie-talkies, USB power banks are a great power source. Here's why:

- They provide a stable 5V output, ideal for many small electronics.
- Convenient to carry, widely available, and rechargeable.
- Most importantly, they come with built-in protection. If you accidentally short the circuit or connect wires the wrong way, they usually just shut off—saving your components from damage.

Designing for Others? You Need Extra Protection

If your circuit might be powered by batteries, solar panels, or other sources that users could easily misconnect, you can't rely on built-in protection alone. Mistakes like reversed polarity or excess current can permanently damage your device. That's where extra protective measures come in.

Properties Meet the eFuse: The Brainy Fuse for Modern Circuits

An electronic fuse (eFuse) is a smart chip that does much more than a traditional fuse. It monitors the power going into your circuit and automatically reacts to dangerous situations:

Overvoltage: Too much voltage? It shuts down.

Undervoltage: Too little voltage? It prevents erratic behavior.

Overcurrent: Drawing too much current (like during a short)? It cuts power.

Overheating: Some eFuses even shut down when they get too hot.

- You can find them under categories like Hot Swap Voltage Controllers on sites like Mouser.
- Setting one up usually involves connecting a few resistors or capacitors around it, depending on the datasheet. These parts help you define exactly what limits the eFuse should enforce—perfect for protecting boards like Arduinos.

What About Reverse Polarity?

- Basic eFuses might not protect your circuit if the power is connected backward. To guard against this, you can:
- Add a P-channel MOSFET to block reverse voltage, or
- Use an advanced eFuse that already includes this feature (though these tend to cost more).

The Bottom Line

Whether you're powering up a hobby project or creating a product for others, eFuses offer peace of mind. They're compact, customizable, and incredibly effective at preventing

common electrical mishaps. Adding one to your design could be the smartest protective step you take.

Summary:

The video explains how to safely power electronic circuits using smart protection methods.

It highlights USB power banks as safe options for personal projects due to built-in safety features.

For more complex or public projects, it recommends using eFuse chips to guard against overvoltage, overcurrent, and other risks.

It also mentions adding extra components like MOSFETs for full reverse voltage protection.

★ Video-49:Everything you need to know when buying /using an Oscilloscope

Understanding Oscilloscopes: A Practical Overview

An oscilloscope is a diagnostic tool that visually displays how electrical signals (typically voltage) change over time. Think of it as a real-time graphing device for electronics.

A Prioritizing Safety

Mains Voltage is Hazardous: Circuits connected directly to wall outlets can be extremely dangerous.

Scope Ground = Earth Ground: The oscilloscope's ground lead is tied to earth ground. Improperly connecting it to a live circuit (especially non-isolated mains) may cause a short circuit, potentially damaging the scope and posing a serious safety risk.

Safe Methods: Use an isolation transformer or a differential probe when working with mains power to avoid accidents.

Selecting the Right Oscilloscope

Channels: Number of signals you can monitor simultaneously (usually 2 or 4).

Bandwidth (MHz): Determines how fast a signal it can handle; higher bandwidth is better for fast signals.

Sampling Rate (MS/s or GS/s): Defines how frequently the signal is sampled; higher rates give more accurate details.

Getting Started with Measurements

Probes: Use these to connect your circuit to the scope. Most have a x1/x10 switch.

- x10 Mode offers better signal integrity and allows higher voltage measurement.
- Ensure the oscilloscope settings match the probe setting to avoid incorrect readings.

Triggering: Lets you stabilize repeating signals on-screen by setting a voltage level that tells the scope when to start displaying the waveform.

Vertical (Voltage) Control: Adjusts signal amplitude scale—controls how tall the waveform appears.

Horizontal (Time) Control: Adjusts time scale—controls how stretched or compressed the signal is over time.

Measurement Tools:

- Automatic Measurements like frequency, voltage peaks, or rise time.
- Cursors for manual point-to-point measurement on the waveform.

Coupling Modes: AC vs DC

DC Coupling: Displays both AC variations and DC offset (the full waveform).

AC Coupling: Removes the DC component, making small signal changes easier to observe—ideal for noise or ripple analysis.

Capturing Specific Events

 Single Trigger Mode: Useful for capturing one-off events like capacitor charging or switch bouncing.

Extra Capabilities to Explore

Current Monitoring: Since scopes measure voltage, current is inferred using a current clamp or by measuring voltage across a known resistor (shunt).

FFT (Fast Fourier Transform): Converts your time-based waveform into a frequency spectrum—great for analyzing signal composition.

@ Final Thoughts

An oscilloscope is more than a screen—it's your window into circuit behavior. From verifying signal integrity to diagnosing issues, it's an essential instrument in any electronics workspace. Just remember, safety is always the first signal to watch.

The video explains how an oscilloscope visualizes electrical signals over time, helping users analyze and troubleshoot circuits.

It highlights key features like triggering, probe settings, and measurement controls.

Safety around high-voltage (mains) circuits is strongly emphasized, especially regarding proper grounding.

It also covers extra functions like FFT and current measurement using clamps or shunt resistors.

★ Video-50:Probably the most used component nobody knows of! TL431Guide!

TL431 - A Flexible Precision Voltage Controller

The TL431 is a highly adaptable electronic component widely used for accurate voltage regulation and control. It acts as a programmable reference device and is often a key player in power supply circuits.

What Makes Up the TL431?

- Inside the TL431, you'll find a combination of essential elements:
- A precision 2.5V internal voltage reference
- A comparator for checking voltage levels
- A transistor, working like a controlled switch
- A diode-like structure to help maintain stability

These internal parts work together to provide precise voltage control capabilities.

Using TL431 as a Voltage Threshold Detector

- One basic use of the TL431 is as a comparator:
- Apply a voltage to the 'Ref' pin.
- It will compare this with its internal 2.5V reference.
- Depending on the result, it either conducts or blocks current, effectively acting like a voltage-sensitive switch.

Acting as a Precision Zener Diode

- When the 'Ref' pin is connected directly to the 'Cathode' pin, the TL431 behaves like a stable 2.5V Zener diode:
- It maintains a fixed 2.5V across itself.
- Offers better precision and temperature stability than regular Zener diodes.

Creating Custom Voltage References

- One of the most powerful features of the TL431 is its ability to act as an adjustable voltage regulator:
- By connecting two resistors (R1 and R2) in a voltage divider to the 'Ref' pin, you can set the output voltage.
- The regulated voltage is given by the formula:

$$Vout = 2.5V \times (1 + R1/R2)$$

Using a potentiometer for one of the resistors allows for easy voltage adjustment.

This makes it extremely useful in applications needing custom reference levels like 5V, 12V, etc.

TL431 in Power Supply Circuits

In Switched-Mode Power Supplies (SMPS), the TL431 plays a key role in the feedback mechanism:

- It monitors the output voltage using a resistor divider.
- If the output voltage shifts, the TL431 senses the deviation.
- It then signals the power supply controller (often via an optocoupler) to make corrections and stabilize the output.

This helps maintain a steady voltage output under varying load conditions.

<u><u><u>&</u>Summary:</u></u>

The TL431 is more than just a voltage reference—it's a versatile control component. Whether used as a comparator, precision Zener, or adjustable regulator, its accuracy and flexibility make it a favorite in power management and control systems.

★ Video-51:This component can control tons of circuits! Digital potentiometer Guide!

Why Manual Knobs Aren't Always Ideal

In many circuits, we use adjustable resistors (called potentiometers) to control things like voltage, light intensity, or sensor sensitivity. They're handy when you set them once and

leave them—but they're not useful when you want the values to change automatically or remotely. That's where the problem begins.

Enter Digital Potentiometers - A Smarter Solution

Digital potentiometers (often called digipots) do the same job as regular potentiometers—but with a twist. Instead of adjusting them by hand, a microcontroller (like an Arduino) can change their resistance through digital signals. This makes it easy to automate settings.

What's Going On Inside a Digipot?

Think of a digital potentiometer as a chain made of many small resistors. Inside the chip, there are tiny switches that connect to different points on this chain. The microcontroller tells the digipot which point to connect to, adjusting the resistance—just like turning a physical knob to a new position.

Types of Digital Pots and How to Control Them

O Simple Ones (like X9C Series):

These are easy to control. You send basic signals—like "increase," "decrease," or "select"—and they do the job. The video showed this using push buttons first to demonstrate the concept.

Advanced Ones (like MCP41HVX1):

Some digipots, especially those that need to work with high voltages, use protocols like SPI (Serial Peripheral Interface) for communication. This takes a little more effort but gives more precision and flexibility.

Things to Keep in Mind Before Using a Digipot

Voltage & Current Limits: Not all digital pots can handle high power. If you exceed their limits, they can burn out—like the first one in the video did. That's why a stronger version (like MCP41HVX1) was used for the LED driver.

Matching Resistance Values: When replacing a physical pot, choose a digital one with a similar total resistance.

Resolution Matters: Digipots adjust in steps (like 100 or 256 levels). These steps aren't perfectly smooth like turning a manual knob, so changes happen in little jumps.

Real-World Use Case: Controlling an LED Driver

In the video, the creator swapped out a regular potentiometer in a boost converter circuit (used to drive a bright LED) and replaced it with a digital one. This allowed an Arduino to adjust the brightness of the LED programmatically—no hands needed!

<u>mal Thoughts</u>

Digital potentiometers are powerful little components that give your microcontroller full control over adjustments that would normally need a screwdriver. Whether you're automating brightness, voltage, or any other setting, digipots unlock a whole new level of smart electronics.

<u>**Summary:**</u>

The video explains how digital potentiometers can replace manual knobs in electronic circuits to allow automatic control using microcontrollers like Arduino. It shows how they work internally using resistor chains and switches. Different types are introduced, from simple button-controlled to SPI-based high-voltage models. A real example demonstrates using a digipot to control an LED driver's brightness automatically.

★ Video-52:Negative voltages are more important than you think! So here is how to make them

Creating Negative Voltage Rails: Practical Techniques Explained

Negative voltages play a crucial role in many electronic circuits, especially those involving operational amplifiers. If you're working with systems requiring both positive and negative supplies, here's a summary of key methods to generate negative voltage from a single or dual power source:

1. Prebuilt Dual Voltage Modules

Concept: Uses a charge pump or dedicated chip to convert a single DC input (e.g., +5V) into dual outputs, such as +12V and -12V.

Upside: Plug-and-play solution with minimal effort.

Limitation: Output current is limited and can introduce electrical noise.

2. Tuning a Standard Boost Converter

Concept: Modify a boost converter by adding a simple charge pump (diodes and capacitors) to create negative voltage.

Upside: DIY-friendly and leverages existing modules.

Limitation: Shares drawbacks like limited current and noise with prebuilt solutions.

3. Center-Tapped Transformer (AC to Dual DC)

Concept: Utilizes an AC transformer with a center tap as ground; AC output is rectified and filtered to get positive and negative DC rails.

Upside: Provides high current with low noise and better stability.

Limitation: Needs AC mains, transformer, and is bulky and costly for compact setups.

4. Virtual Ground via Resistor Divider

Concept: Two equal resistors across a DC supply form a midpoint acting as a virtual ground, effectively splitting voltage.

Upside: Extremely simple and cost-effective.

Limitation: Poor current capacity, voltage drift if current draw is uneven.

Tip: Using a buffer op-amp at the midpoint helps maintain virtual ground stability under load.

Conclusion:

Each method involves trade-offs among cost, complexity, current capability, and noise. Selection depends on your specific application and design constraints.

Summary :

The video explains how to create a dual power supply that provides both positive and negative voltages from a single source. It highlights the importance of negative voltages in circuits like op-amps and audio amplifiers. Several practical methods are demonstrated, including modules, converters, transformers, and virtual grounds. The pros and cons of each approach are also discussed.

★ Video-53:Mechanical switch are obsolete? Switch to a Latch Circuit

Ditch the Switch: Embracing Latch Circuits for Smarter Control

Overview: Latch circuits are electronic systems that can store a state—either ON or OFF—even after the activating input signal is removed. This makes them a powerful alternative to traditional mechanical switches.

1. What is a Latch Circuit?

A latch circuit is a type of memory element that changes its output based on input signals and then retains that state until told otherwise. Unlike standard switches, it doesn't require a continuous input to stay active.

2. How It Works:

Latch circuits generally have two key inputs:

- SET Activates or turns the output ON.
- RESET Deactivates or turns the output OFF.

A brief pulse to either input is enough to change the output state, making them ideal for momentary controls.

3. Practical Applications:

Latch circuits are found in many real-world devices where a short action results in a long-lasting effect. Examples include:

- Power buttons on electronics that stay on until pressed again.
- Latching relays in corridor lighting that toggle with each press.

- Safety systems like overcurrent protection that stay OFF until reset.
- Power-saving circuits where a microcontroller shuts itself down.

4. Building a Latch:

With Logic Gates: A simple SR latch can be built using two NOR or NAND gates wired in a cross-connected configuration.

With Discrete Components: You can create toggle latches using transistors (BJTs or MOSFETs), resistors, and capacitors. These toggle ON with one button press and OFF with the next.

5. Benefits Over Mechanical Switches:

- Greater design flexibility and functionality.
- Potentially lower cost when customized.
- Ability to handle specific voltage/current demands.
- Seamless integration into digital and automated systems.

Conclusion:

Latch circuits are fundamental for creating electronic memory and persistent states using basic components. They're a smart upgrade from mechanical switches in modern electronic designs.

∠Summary:

The video explains how latch circuits can hold an ON or OFF state even after the input signal is removed. It covers their basic operation using SET and RESET inputs. Practical uses include power buttons, safety systems, and power-saving circuits. It also shows how to build latches using logic gates or simple electronic components.

Video-54:The best protection for your circuit is Not a Fuse!...But a Resetable Fuse

Why Traditional Fuses Aren't Always the Best Choice

When designing electronic circuits, things can go wrong—like a short circuit—causing too much current to flow. This can permanently damage components unless there's a way to stop it in time.

<u>XX</u> Classic Glass Fuses – Simple but Disposable

Glass fuses have a thin wire inside that melts when the current is too high. This stops the flow of electricity, protecting your circuit. However, once blown, they can't be reused—you have to replace them, which becomes inconvenient and costly over time.

😘 Smarter Protection: Self-Resetting Fuses (PPTCs)

- A better alternative is the resettable fuse, technically called a PPTC (Polymeric Positive Temperature Coefficient). These act like automatic circuit breakers:
- When too much current flows, they heat up.
- As they get hotter, their resistance increases drastically, limiting current flow and shielding your components.
- After the issue is resolved and they cool down, they reset themselves and return to normal operation—no need to replace anything!

Key Things to Understand About PPTCs

Hold Current (I_hold): The safe current it can pass without activating.

Trip Current (I_trip): The current level where the PPTC will definitely start blocking current.

Max Voltage & Max Current: Exceeding these can destroy the device, so stay within the specs!

Reaction Time: Not as fast as some traditional fuses, but still effective, especially for moderate overcurrent.

Residual Current: When tripped, they don't block 100% of the current—a small flow remains to keep them in a tripped state.

Resistance Drift: After multiple trips, they might not fully return to their original low-resistance state.

Best Use Cases for Resettable Fuses

PPTCs are ideal for places where replacing fuses is a hassle—like in battery-powered gadgets, USB ports, LED setups, small motors, or DIY electronics. They're cheap, compact, and reliable for general-purpose protection.

Bottom Line

Resettable fuses are clever protectors for your electronics. They react to danger by getting hot and limiting current, then recover automatically—offering long-term, reusable safety without manual maintenance.

Summary:

• The video explains that traditional fuses protect circuits but need replacement after tripping.

- Resettable fuses (PPTCs) offer reusable protection by increasing resistance when overheated.
- They automatically reset once the fault is cleared and the device cools down.
- PPTCs are ideal for hobby electronics where convenience and reusability matter.

★ Video-55:The most important circuit for our Electrical Future

Making Electronics Grid-Friendly: The Role of Power Factor Correction (PFC)

In today's electrical landscape, not all electronic devices interact with the power grid equally. Some are considered "grid-friendly," while others can be problematic.

Understanding Grid-Friendly vs. Harmful Devices

Grid-Friendly Devices: These draw power in a clean, sinusoidal pattern that's synchronized with the grid voltage. For example, resistive loads like heaters operate this way, maintaining harmony between current and voltage.

Problematic Devices: Many modern electronics, such as inexpensive LED drivers or poor-quality adapters, draw power in sharp, erratic bursts. Their current is often out of phase with the voltage, disrupting grid efficiency.

Breaking Down Power Types

Electric power can be viewed in three categories:

1. Real Power (Watts) – This is the usable energy a device consumes to perform work, like lighting a bulb. It's the "substance" of power.

- **2. Apparent Power (Volt-Amps) –** The total power the grid delivers, combining both useful energy and losses. It's like pouring soda with foam both the drink and foam take up space.
- **3. Reactive Power (Volt-Amps Reactive) –** This doesn't contribute to useful work but still affects the grid. It's the "foam" in the glass, wasting space and capacity.

The Importance of Power Factor

- The Power Factor (PF) indicates how efficiently a device uses power. A PF close to 1 means most of the supplied power is doing useful work — minimal waste.
- Devices with a low PF burden the grid with excess reactive power, leading to inefficiency and potential overloads.

Solving the Problem: Power Factor Correction (PFC)

To address low power factor issues, we use PFC techniques:

Passive PFC: Involves basic components like inductors and capacitors to correct minor phase imbalances. It's commonly used in simpler systems like motor circuits.

Active PFC: A more sophisticated method, it employs electronic control (often a boost converter) to reshape the current draw. This smoothens current spikes and aligns it with the voltage waveform, greatly improving PF in devices prone to harmonic distortion.

Conclusion

Power Factor Correction transforms inefficient, grid-unfriendly devices into systems that consume power more cleanly and responsibly. As our reliance on electronics grows, PFC becomes essential to ensure a stable, efficient, and sustainable power grid.



The video explains how some electronic devices draw power in a way that stresses the power grid, while others work in harmony with it. It introduces the concepts of real, apparent, and reactive power. A low power factor means more wasted energy and strain on the grid. Power Factor Correction (PFC), especially active PFC, helps devices draw power more efficiently and cleanly.

Video-56:These 3 cent component are actually useful?(color ring inductor)

<u>Are Those Color-Banded Inductors Actually Any Good? — A Closer Look</u> #Overview:

This discussion revolves around those small, resistor-like components with colored bands — color-coded inductors. Though they appear similar to resistors, they function as inductors. The big question is: Are these ultra-cheap components reliable or just hobby-grade toys?

#Different Flavors of Inductors

The video starts by distinguishing between several common types of inductors:

Power Inductors (Toroidal & SMD):

• These are often used in power regulation circuits. Toroidal types are recognizable by their donut-shaped cores wrapped in copper wire. SMD (Surface-Mount Device) inductors are smaller and typically found on compact circuit boards.

Color-Banded Inductors:

 These resemble resistors but are inductors in disguise. They use color bands to indicate inductance, following a code similar to resistors. However, the similarities end there.

The Hidden Pitfalls of Budget Inductors

Despite being popular for their affordability and wide availability, color-ring inductors come with a major downside — a serious lack of technical data. Critical specs, like saturation current, are often not provided, which can lead to poor performance in real-world circuits.

#Understanding Saturation Current

Inductors rely on magnetic fields to function. But there's a limit to how much magnetic energy their cores can store. Once that threshold is exceeded — a point known as core saturation — the inductor essentially stops working as an inductor and behaves more like a resistor. This is dangerous in power electronics, where stable inductance is key to performance.

Real-World Test: Boost Converter Comparison

In a hands-on experiment, a $22\mu H$ color-ring inductor was used in a boost converter circuit and compared to a professionally-rated SMD inductor of the same value.

#Results:

- With the SMD inductor, the converter handled up to 1 Amp of output current stably.
- With the color-ring inductor, the converter output became unstable after 0.5 Amps.

Further testing revealed:

• The SMD inductor reached saturation at ~4 Amps

The color-ring version saturated at just ~1.6 Amps

#Why Datasheets Matter

Professional-grade inductors are sold with datasheets detailing their key specifications — including saturation current, DC resistance, and frequency response. These values are crucial for designing dependable circuits. In contrast, most cheap inductors lack this transparency, making them unreliable for anything beyond experimentation.

Final Thoughts: When (and When Not) to Use Them

Color-coded inductors are fine for:

- Low-current circuits
- Signal filtering
- Oscillators
- Educational use or early-stage prototyping

But for power circuits, especially those involving switching regulators or converters, relying on them is risky. Knowing only the inductance value isn't enough — saturation current and other specs are just as essential.

The video explains that color-ring inductors, though cheap and common, often lack important specs like saturation current. It shows that these inductors saturate earlier than proper SMD inductors, causing poor performance in power circuits. Testing reveals they're only suitable for low-current or simple applications. For reliable power designs, inductors with detailed datasheets are essential.

★ Video-57: Ground is more important than you think

#Why Grounding Matters More Than You Realize

1. The Earth as a Natural Electrical Reservoir:

The soil beneath our feet isn't just dirt—it can conduct electricity. Because the Earth is so vast, it acts like a huge stable electrical reference point with almost unlimited capacity to absorb or release electrons. This makes it a natural "zero voltage" baseline for electrical systems.

2. Safety Grounding in Homes:

The green/yellow wire you see in power plugs is the safety ground, often called Protective Earth (PE). It connects the metal body of appliances to the Earth. If a live wire inside the appliance accidentally touches the casing, this safety ground offers a direct path for dangerous current to flow, triggering circuit breakers or residual current devices to quickly cut off power. This mechanism protects you from potentially fatal electric shocks.

3. Preventing Static Charge Hazards:

Static electricity can build up on objects (like when you shuffle on carpet and then feel a zap). Grounding these objects allows the static charge to safely dissipate into the Earth. This is essential both for protecting delicate electronic devices from damage and for avoiding sparks that could ignite flammable materials.

4. Circuit Ground in Electronics:

In electronic schematics and circuit boards, the symbol "GND" refers to the common reference point or 0-volt line within that specific system. Although this circuit ground may not always connect physically to the Earth, it functions as the baseline "ground" for all signals in the device, helping maintain consistent voltage levels and stable operation.

<u>summary:</u> "Ground" can mean different things depending on context: the planet Earth itself, a critical safety wire in electrical installations, or a reference point in electronic circuits. All these forms of grounding are fundamental to safe, reliable, and effective electrical and electronic operation.

★ Video-58:This component solves "All" Motor Problems? (Motor Encoder)

#Understanding Motor Encoders: The Key to Precise Motor Control

Motor encoders are specialized sensors that help a microcontroller (like an Arduino) understand exactly how much a motor shaft has turned and in which direction. This feedback is essential for precise motor operation.

#Types of Motor Encoders

1. Basic Mechanical Rotary Encoders

These encoders use a rotating disc embedded with a metal pattern. Two contact pins (often labeled A and B) slide over this pattern and generate electrical signals as the disc spins. The sequence of these signals determines the motor's direction of rotation. While simple and

cost-effective, these encoders offer limited resolution, making them less suitable for applications that require high precision.

2. Magnetic Encoders (e.g., AS5600 sensor)

Magnetic encoders provide a much more accurate solution. A small magnet attached to the motor shaft spins along with it, and the encoder chip uses Hall effect sensors to detect the magnet's position. This setup can deliver very high resolution, often thousands of steps per revolution, enabling extremely precise motor feedback.

#Why Motor Encoders Are Essential?

Synchronizing Multiple Motors

 When using more than one motor, such as in robots, each motor might spin at slightly different speeds even if powered equally. Encoders allow the controller to monitor the exact speed and position of each motor, enabling real-time adjustments so both motors operate in perfect harmony.

Advanced Control for BLDC Motors

 Brushless DC motors (BLDC) benefit greatly from encoders, as they allow near stepper-like precision in controlling speed and position. This makes them ideal for applications that demand exact movements—like 3D printers or robotics. Dedicated motor controllers can use encoder data to optimize performance and efficiency.

<u>**<u><u></u><u><u></u><u><u></u><u><u></u><u><u></u><u>Summary:</u></u></u>**</u></u></u></u>

In essence, motor encoders turn a motor's mechanical rotation into valuable digital feedback. This feedback transforms simple motors into smart devices capable of precise speed and position control, enabling smoother operation and better performance across a variety of uses.

★ Video-59:This \$0.70 Component saves your circuit

#How a \$0.70 Component Can Shield Your Circuit from Voltage Surges

Electronics are vulnerable to sudden voltage spikes caused by events like lightning strikes, static electricity, or the switching of heavy electrical loads. These unexpected surges can easily damage or destroy delicate circuits.

To guard against these threats, engineers use specialized components designed to absorb or divert excess voltage quickly and safely:

1. TVS Diodes (Transient Voltage Suppressors):

These tiny devices react almost instantly—within trillionths of a second—to voltage spikes. When a surge occurs, a TVS diode creates a low-resistance path that redirects the harmful energy safely to ground, typically dissipating it as heat. They're ideal for protecting sensitive, low-voltage electronics against fast, transient spikes.

2. MOVs (Metal Oxide Varistors):

MOVs usually appear as small, disc-shaped parts, often blue. Under normal conditions, they act like insulators with very high resistance. But when a high-voltage surge hits, their resistance suddenly drops, allowing them to shunt the excess energy away from the circuit. While slightly slower to respond than TVS diodes, MOVs can handle larger amounts of energy and are commonly found in power supply circuits.

3. GDTs (Gas Discharge Tubes):

Inside these tiny tubes is a special gas that becomes conductive during very high voltage spikes, such as those caused by lightning. When triggered, the gas "sparks" and safely channels the surge current to ground. Although GDTs react slower than TVS diodes or MOVs, they're capable of handling extremely large surge currents, making them suited for heavy-duty protection.

Testing shows that TVS diodes and MOVs can effectively shield even simple circuits, like a blinking LED, from strong electrostatic discharge pulses. However, GDTs may require higher trigger voltages, limiting their use in low-voltage applications.

Choosing the right surge protection device depends on how quickly it must react and how much energy it needs to absorb. Higher-end protectors often combine multiple technologies and safety features (like fuses or thermal cutoffs) to handle bigger surges more reliably—explaining their higher price.

≤Summary:

The video explains how sudden voltage spikes from lightning, static electricity, or heavy load switching can damage circuits. It introduces three key surge protection components: TVS diodes, MOVs, and GDTs. Each component varies in response speed and energy handling capabilities. The video demonstrates how these devices protect circuits from high-voltage surges effectively.

★ Video-60:Is this the NEW GOLDEN standard for communication? (I3C)

Crafting an Affordable Haptic Driver Breakout Board

The video focuses on building a cost-effective vibration device controller (haptic feedback) by creating a custom breakout board for the BOS1921 chip. While the official test board costs around €240, the chip itself is only about €4. The creator's goal was to design a much cheaper alternative to integrate this chip into projects.

#Steps to Build the Custom Board

1. Research & Planning

The creator studied the chip's datasheet and the official expensive board's manual to understand the necessary circuit and design details.

2. Designing the Circuit & PCB

A detailed schematic was drawn first, followed by designing a compact four-layer PCB layout to fit all components efficiently.

3. Component Assembly

Solder paste was applied, and all tiny components carefully positioned. Using a mini hot plate, the solder was melted to secure the parts.

4. Debugging Issues

Initial testing showed the board getting unusually hot. Thermal imaging revealed a capacitor was installed backwards, with the positive terminal incorrectly placed. After correcting this, the board functioned flawlessly.

5. Final Outcome

The finished board works perfectly and cost just around €10 to make, a fraction of the official test board price.

Exploring 13C: The Next-Gen Communication Protocol

The BOS1921 chip supports both traditional I2C communication and a newer, faster protocol called 13C. This video explores the key differences between these two communication standards.

#Comparing 13C vs. I2C

Data Transfer Speed:

 13C can achieve speeds up to 12.5 Mbps, significantly faster than I2C's typical 1 Mbps.

Power Efficiency:

• I2C relies on "open-collector" drivers needing pull-up resistors, which can slow communication and consume more power. 13C uses "push-pull" drivers, making it faster and more energy-efficient.

Addressing Devices:

• I2C devices usually have fixed addresses, risking conflicts if two devices share the same address. 13C automatically assigns unique addresses to prevent conflicts.

Common Command Codes (CCC):

• 13C includes built-in commands for standard operations like resetting addresses, simplifying device management.

Advanced Features:

 Though not fully supported by the BOS1921, 13C can enable hot-joining devices (adding/removing devices without rebooting) and in-band interrupts (signaling without extra wires).

Implementation Complexity:

 I2C is simpler and often implemented via software ("bit-banging"). In contrast, 13C requires dedicated hardware support in microcontrollers, which is not yet widespread.

#Takeaway

The custom-made breakout board dramatically cuts costs while delivering full functionality for the BOS1921 haptic chip. Although 13C offers notable improvements in speed and efficiency over I2C, its complexity and limited hardware support mean I2C remains widely used, even on official test equipment. The future may see broader adoption of 13C as hardware support grows.

The video shows how to build a low-cost breakout board for the BOS1921 haptic chip, replacing an expensive official test board. It details the design, assembly, and troubleshooting process. It also introduces 13C, a new communication protocol faster and more efficient than I2C. Finally, it compares 13C's advantages and complexities, highlighting its potential despite limited current hardware support.

★ Video-61:The world's simplest Audio Amp just got better?(MOSFET Amp)

#Improving a Basic Audio Amplifier: From Simple to Stronger

A popular "world's simplest" audio amplifier using a BJT transistor works well for headphones but lacks the power to drive larger speakers. Plus, with many modern phones dropping headphone jacks, a stronger, wired amplifier becomes more useful.

The Challenge: Boosting Power for Bigger Speakers

The original BJT transistor (like the BC337) can't supply enough current for loudspeakers. The goal is to upgrade the amp to push more current through the speaker without distortion or overheating.

Upgrade Attempt 1: Switching to a Darlington Transistor

Replacing the small BJT with a TIP142 Darlington transistor allows more current handling.

Issues & Fixes:

- The Darlington needs a higher voltage to operate cleanly, so the supply voltage is raised from 5V to 12V.
- Higher currents cause resistors to heat up, so they are swapped for power resistors.
- The transistor itself gets hot, requiring a heatsink.

This upgrade delivers louder sound and manages the heat, resulting in a practical improvement.

Upgrade Attempt 2: Using a MOSFET (IRFZ44N)

MOSFETs are voltage-controlled and have very low on-resistance, so they waste less voltage and heat than BJTs.

Key Points:

- Similar setup with power resistors and heatsink.
- Potentially louder output due to lower voltage drop.

Biasing the MOSFET gate is critical and done via a potentiometer to minimize distortion.

Comparing Audio Quality and Efficiency

Using an oscilloscope and FFT analysis reveals:

- The Darlington amp produces cleaner, less distorted sound, closer to the original signal.
- The MOSFET amp, though efficient and simpler, introduces more harmonic distortion in this Class A configuration.

Final Thoughts

For simple Class A audio amps, BJTs (especially Darlingtons) typically offer better sound fidelity despite being less efficient and generating more heat. MOSFETs excel in switching and efficiency but may introduce distortion in this basic amp design. Overall, these simple amps are quite inefficient, regardless of transistor type.

≤Summary:

The video shows how to upgrade a simple headphone amplifier to drive louder speakers by increasing current capacity. It first replaces the original BJT with a Darlington transistor, improving power but needing higher voltage and cooling. Then, it tries a MOSFET for better

efficiency and lower voltage drop but finds more distortion. Overall, the Darlington gives cleaner sound, while the MOSFET is more efficient but less linear in this setup.

★ Video-62:Not a Microcontroller!....This is better!?

Why Choose a PLC Over a Microcontroller? Understanding Industrial Automation with Arduino Opta

This video dives into the world of PLCs (Programmable Logic Controllers) by demonstrating how an Arduino Opta PLC automates a small conveyor belt system.

#What Makes PLCs Special?

PLCs are rugged, purpose-built mini-computers designed for controlling machines and industrial processes. Unlike typical hobbyist microcontrollers such as Arduino or ESP boards, PLCs are engineered to thrive in demanding environments.

Key Advantages of PLCs:

- **Industrial-Grade Durability:** PLCs can handle higher voltages (commonly 24V for inputs) and directly control powerful devices like motors or large lights at 250V AC through integrated relays.
- Standardized Connectivity: Inputs and outputs follow industrial wiring standards, usually featuring screw terminals for reliable and easy connections to sensors and actuators.

- **Simplified Logic Programming:** PLCs often use graphical programming languages (like function block diagrams), allowing users to visually design control logic. This method is often faster and more intuitive than writing complex lines of code.
- **Real-Time Monitoring:** PLC software typically offers live debugging, enabling users to watch the program's behavior as it runs, which helps quickly identify and fix issues.

#Comparing PLCs to Microcontrollers:

- **Microcontrollers** are budget-friendly and highly flexible, ideal for custom and specialized applications. However, they usually require additional circuitry to manage high voltages or heavy loads safely.
- **PLCs** offer a plug-and-play experience with industrial hardware, boasting robustness and standardized interfaces. They tend to be more expensive and might not match microcontrollers in high-speed or ultra-specific control tasks.

Example: Controlling a Conveyor Belt with Arduino Opta PLC

- **Inputs:** Start/Stop buttons and proximity sensors (including metal detection).
- **Outputs:** Motor to drive the belt and indicator lights (red/green).
- **Logic:** When a metal object is detected, the PLC stops the belt, reverses it briefly to eject the object, and then resumes normal operation.

In essence, PLCs are the reliable, industrial-strength brains designed for smooth automation in factories and similar environments, while microcontrollers offer customizable, cost-effective solutions for tailored or high-speed projects. Both have their place depending on the application.



The video explains what a PLC (Programmable Logic Controller) is and how it differs from regular microcontrollers like Arduino. It shows how an Arduino Opta PLC can automate a mini conveyor belt using buttons, sensors, and motors. The video highlights PLCs' industri durability, easy wiring, and graphical programming for control logic. It also compares PLCs and microcontrollers, emphasizing their strengths in different automation tasks.